

06 FEB 2023

Reg. No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

(COB)

Question Paper Code	11683
---------------------	-------

B.E./B.Tech. - DEGREE EXAMINATIONS, NOV/DEC 2022
 Third Semester
Electrical and Electronics Engineering
20EEPC301 - ANALOG ELECTRONICS
 (Regulations 2020)

Duration: 3 Hours


Max. Marks: 100

PART - A (10 × 2 = 20 Marks)
 Answer ALL Questions

- | | <i>Marks,
K-Level,CO</i> |
|--|------------------------------|
| 1. Compare BJT and FET. | 2,K1,CO1 |
| 2. Mention the four different configuration of Differential amplifier. | 2,K1,CO1 |
| 3. Define CMRR for a differential amplifier. What is the value for the ideal case? | 2,K1,CO2 |
| 4. Differentiate oscillator and amplifier. | 2,K2,CO2 |
| 5. In practical op-amps, what is the effect of high frequency on its performance? | 2,K2,CO3 |
| 6. What happens when the common terminal of V+ and V-sources is not grounded? | 2,K1,CO3 |
| 7. What is a sample and hold circuit? Where is it used? | 2,K1,CO4 |
| 8. List the various A/D conversion techniques. | 2,K1,CO4 |
| 9. Mention the applications of 555 timer. | 2,K1,CO5 |
| 10. Define load regulation. | 2,K1,CO5 |

PART - B (5 × 13 = 65 Marks)
 Answer ALL Questions

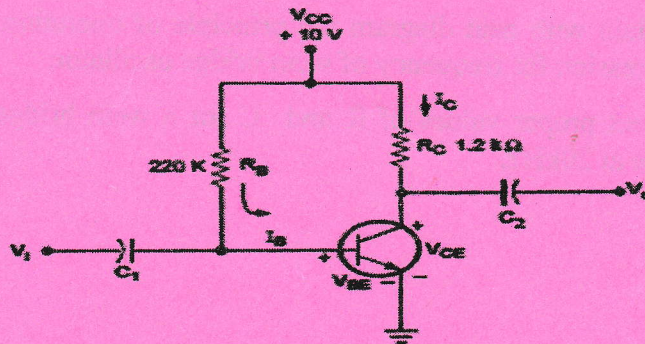11. a) Explain the DC and AC load line analysis of BJT 13,K2,CO1
- OR**
- b) For the circuit shown, find I_B, I_C, V_{CE}, V_C & V_{BC} for $V_{BE}=0.7$ and $\beta=50$. 13,K2,CO1



K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

11683

12. a) Describe the working of class A and class B power amplifier in detail with relevant diagram. 13,K2,CO2

OR

- b) Derive the expression and characteristics of RC phase shift oscillator. 13,K2,CO2

13. a) With a neat circuit diagram & equation discuss the operation of inverting and non-inverting summer. 13,K3,CO3

OR

- b) Discuss in detail about the DC characteristics of op-amp. 13,K3,CO3

14. a) With a help of neat diagram explain the working principle of an instrumentation amplifier using op-amp. 13,K2,CO4

OR

- b) Explain the R-2R ladder type D/A converter with necessary equations. What are the advantages of R-2R ladder type D/A? 13,K2,CO4


15. a) Draw and explain the functional block diagram of astable multivibrator using a 555 timer. Derive the expression for time delay. 13,K2,CO5

OR

- b) Draw and explain the functional block diagram of 723 regulators. 13,K2,CO5

PART C (1 × 15 = 15 Marks)

16. a)

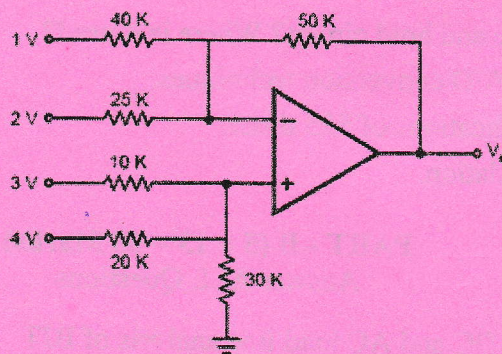

15,K3,CO3

Find V_o for the circuit.

OR

- b) (i) Explain with neat diagram the principle of operation and derive the expression for frequency of wein bridge oscillator. 10,K2,CO2

(ii) Select proper values of R and C for a wein bridge oscillator to oscillate at 20kHz. 5,K2,CO2