

15 FEB 2023

Reg. No.

Question Paper Code

11720

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV/DEC 2022

Third Semester

Electronics and Instrumentation Engineering

(Common to Instrumentation and Control Engineering)

20EIPC303 - ANALOG ELECTRONIC CIRCUITS

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

- | | <i>Marks,
K-Level,CO</i> |
|---|------------------------------|
| 1. What is depletion region in PN junction diode? | 2,K1,CO1 |
| 2. What is diffusion current? | 2,K1,CO1 |
| 3. Differentiate FET and MOSFET. | 2,K2,CO2 |
| 4. List the advantages of push pull amplifier. | 2,K2,CO2 |
| 5. Define Amplification factor in JFET. | 2,K1,CO3 |
| 6. What is crossover distortion in a power amplifier and how to eliminate it? | 2,K1,CO3 |
| 7. List the effect of negative feedback on the noise and bandwidth of an amplifier. | 2,K1,CO4 |
| 8. Define piezoelectric effect. | 2,K1,CO4 |
| 9. Mention the characteristics of an ideal op amp. | 2,K1,CO5 |
| 10. Differentiate between open loop gain and closed loop gain. | 2,K1,CO5 |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Explain the construction of PN junction diode and explain the operation of it with V-I characteristics curve. 13,K2,CO1
- OR**
- b) Explain the working principle and application of SCR. 13,K2,CO1
12. a) Explain the construction and operation of depletion mode MOSFET and draw its characteristics. 13,K2,CO2
- OR**
- b) Explain the push pull class B power amplifier and write its application. 13,K2,CO2

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

11720

13. a) Explain the voltage series feedback amplifier circuit and find the gain and impedances. 13,K2,CO3

OR

b) Explain the working principle and application of Colpitts oscillator. 13,K2,CO3

14. a) Explain how an op-amp can be used as integrator and derive the expression for output voltage. 13,K2,CO4

OR

b) Explain the differential amplifier with neat circuit diagram. 13,K2,CO4

15. a) Explain how a 555 timer can be used as Astable oscillator. 13,K2,CO5

OR

b) Explain the principle and operation of Voltage regulator IC. 13,K2,CO5

PART - C (1 × 15 = 15 Marks)

16. a) Explain the input characteristics and output characteristics of a NPN transistor in CE configuration and compare it with CB and CC configurations. 15,K2,CO1

OR

b) Explain the modeling of BJT into hybrid model and find the input output parameters when it is used as an amplifier. 15,K2,CO2