

12 8 FEB 2023

Reg. No. []

Question Paper Code 11737

B.E/B.Tech - DEGREE EXAMINATIONS, NOV/DEC 2022
Semester

Information Technology

(Common to Computer Science and Engineering & M.Tech. - Computer Science and Engineering)

20ESIT203 - DIGITAL PRINCIPLES AND SYSTEM DESIGN
(Regulations 2020)

Duration: 3 Hours


Max. Marks: 100

PART - A (10 × 2 = 20 Marks)
Answer ALL Questions

- | | <i>Marks,
K-Level,CO</i> |
|--|------------------------------|
| 1. Implement AND gate using only NOR gate. | 2,K1,CO1 |
| 2. Find the octal and binary equivalent of hexadecimal numbers AB.CD. | 2,K1,CO1 |
| 3. Design the combinational circuit with 3 inputs and 1 output. The output is 1 when the binary value of the input is less than 3 and the output is 0 otherwise. | 2,K2,CO2 |
| 4. Distinguish between combinational logic circuit and sequential logic circuit. | 2,K2,CO2 |
| 5. Differentiate Mealy circuit and Moore circuit. | 2,K2,CO3 |
| 6. Write the characteristics table and excitation table of SR flipflop. | 2,K1,CO3 |
| 7. Write the HDL code for Half adder using gate level modeling. | 2,K1,CO4 |
| 8. What is Verilog? What are the different types of Modeling? | 2,K1,CO4 |
| 9. Compare SRAM and DRAM. | 2,K1,CO6 |
| 10. A seven bit Hamming code is received as 1111110. What is the correct code? | 2,K1,CO6 |

PART - B (5 × 13 = 65 Marks)
Answer ALL Questions

 11. a) Simplify the following functions using K-map technique 13,K2,CO1
(i) $G(A,B,C,D) = \sum m(0,1,3,7,9,11)$.
(ii) $f(w,x,y,z) = \sum m(0,7,8,9,10,12) + \sum d(2,5,13)$.
- OR**
- b) (i) Express the following function in sum of min-terms and product of max-terms $F(X,Y,Z) = X + YZ$ 7,K2,CO1
(ii) Convert the following logic system into NAND gates only. 6,K2,CO1



12. a) Design a logic circuit that accepts a 4 bit Gray code and converts it into 4 bit binary code. 13.K2,CO2


OR

- b) (i) Realize 4 x 16 decoder using 3 x 8 decoders with enable input. 6.K2,CO2
 (ii) Implement the following functions using a 4*1 multiplexer. 7.K2,CO2
 $F(W,X,Y,Z) = \sum m(0,1,3,4,8,9,15)$.

13. a) Design a modulo 5 synchronous counter using JK Flip Flop and implement it. 13.K2,CO3

OR

 - b) Design a sequential circuit by the following state diagram using T-flip flops. 13.K2,CO3



14. a) Write behavioural VHDL Description of 8 bit shift register with direct reset 13.K2,CO4

OR

- b) Design a 2-bit magnitude comparator and write a verilog HDL code 13.K2,CO4

15. a) Implement the switching functions. 13.K2,CO6

$$Z1 = ab'd'e + a'b'c'd'e' + bc + de$$

$$Z2 = a'c'e$$

$$Z3 = bc + de + c'd'e' + bd$$

$$Z4 = a'c'e + ce$$

using 5 x 8 x 4 PLA

OR

b) Implement the following function using PAL

13,K2,CO6

$$F1(A, B, C) = \Sigma(1, 2, 4, 6);$$

$$F2(A, B, C) = \Sigma(0, 1, 6, 7);$$

$$F3(A, B, C) = \Sigma(1, 2, 3, 5, 7).$$

PART - C (1 × 15 = 15 Marks)

16. a) Design an asynchronous sequential circuit with 2 inputs X and Y and one output Z. Whenever Y is 1, input X is transferred to Z. When Y is 0; the output does not change for any change in X. Use SR latch for implementation of the circuit. 15,K2,CO5

OR

b) Design an asynchronous sequential circuit with inputs x1 and x2 and one output z. Initially and at any time if both the inputs are 0, output is equal to 0. When x1 or x2 becomes 1, z becomes 1. When second input also becomes 1, z=0; the output stays at 0 until circuit goes back to initial state. 15,K2,CO5