

12. a) Explain the operation of single phase fully controlled bridge converter fed dc drive and draw its waveform. 13,K2,CO2
- OR**
- b) Explain the operation of four-quadrant chopper fed DC separately excited motor drive with power circuit. 13,K2,CO2
13. a) Describe the operation of variable frequency control of three phase VSI fed induction motor drive with necessary diagram. 13,K2,CO3
- OR**
- b) A 3-phase, 60 Hz, 8 pole wound rotor induction motor is controlled using slip power recovery scheme. The open circuit line voltage is 1800V. If the motor has to develop 800 kW at a speed of 700 RPM, calculate (i) slip power (ii) DC line voltage (iii) DC line current. 13,K3,CO3
14. a) Explain self-control technique of synchronous motor with constant margin angle control. 13,K2,CO4
- OR**
- b) With neat block diagram, explain the operation of separate-controlled mode of synchronous motor. 13,K2,CO4
15. a) Explain in detail the design of current controller of closed loop speed control system of DC separately excited motor. 13,K2,CO5
- OR**
- b) Derive the transfer function of DC motor load system with armature voltage control. 13,K3,CO5

PART - C (1 × 15 = 15 Marks)

16. a) (i) Explain the operation of a 'Power factor control' based self – controlled synchronous motor drive. 8,K2,CO4
 (ii) Derive the transfer function of the power converter of a dc motor load system with a neat diagram. 7,K3,CO4
- OR**
- b) (i) Explain open loop V/F speed control of synchronous motor with a neat diagram. 8,K2,CO4
 (ii) Describe the closed loop speed control of separately excited DC motor by proportional Controller. 7,K2,CO5