

Reg. No.

Question Paper Code

11976

10 JUL 2023

M.E. / M.Tech. - DEGREE EXAMINATIONS, APRIL/MAY 2023

Second Semester

M.E. – Power Electronics and Drives

20PPEPC202 – SOLID STATE DC DRIVES

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

- | | <i>Marks,
K-Level,CO</i> |
|--|------------------------------|
| 1. Compare the constant torque and constant power operation of the DC motor | 2,K2,CO1 |
| 2. Draw the speed -torque characteristics of DC motor. | 2,K2,CO1 |
| 3. Write the importance of freewheeling diode in the converter circuits. | 2,K1,CO2 |
| 4. How to implement braking in DC controlled drives? | 2,K2,CO2 |
| 5. Draw the diagram of class E chopper controlled drive. | 2,K2,CO3 |
| 6. List the applications of Chopper fed DC drives. | 2,K1,CO3 |
| 7. Write the key considerations when modeling the power converters using a linear transfer function approach. | 2,K1,CO4 |
| 8. Enlist the sensing and feedback elements used in the DC drives. | 2,K1,CO4 |
| 9. Compare the performance of a micro-computer controlled DC drive using a Phase Locked Loop with a traditional analog control system. | 2,K2,CO5 |
| 10. Write the disadvantages of analog control of electrical drives. | 2,K1,CO5 |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Explain any two methods of speed control in DC motor. 13,K2,CO1
- OR**
- b) Explain Constant torque operation of DC motor. 13,K2,CO1
12. a) (i) A separately excited dc motor operating from a single phase half controlled bridge at a speed of 1400rpm has an input voltage of $330\sin 314t$ and a back emf of 80v. The SCRs are fired symmetrically at $\alpha=30$ in every half cycle. The armature has a resistance of 4Ω . Calculate the average armature current and the motor torque. 6,K2,CO2
- (ii) Explain the different power factor improvement methods in single phase converters 7,K2,CO2

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

11976

OR

- b) Explain the motor performance parameters and input supply performance parameters of Single Phase DC Drives. *13,K2,CO2*

13. a) Explain the non-circulating current and circulating current mode of operation of Three phase Dual converters. *13,K2,CO3*

OR

- b) Explain the operation of class D chopper controlled DC Separately excited motor with waveforms. *13,K2,CO3*

14. a) Explain in detail the design of current controller of closed loop control system of dc separately excited dc motor. *13,K2,CO4*

OR

- b) How does the simulation of a chopper-fed DC drive differ from a converter-fed DC drive, and what are the specific challenges involved. *13,K2,CO4*

15. a) Explain with a program flow chart the load distributed operation micro computer control of dc drive. *13,K2,CO5*

OR

- b) Explain the phase locked loop control of DC drives with program and flowchart for constant horse power operation. *13,K2,CO5*

PART - C (1 × 15 = 15 Marks)

16. a) Compare different current sensing techniques, such as shunt resistors, Hall effect sensors, and current transformers. Evaluate their advantages, disadvantages, and suitability for different motor types. *15,K3,CO5*

OR

- b) Design a micro-computer control system for a DC drive using a Phase Locked Loop. Consider the specifications such as speed regulation, torque control, and response time. *15,K3,CO5*