

Reg. No.

Question Paper Code

12137

11 AUG 2023

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2023

Second Semester

Civil Engineering

20ESEE202 - BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)


Answer ALL Questions

- | | <i>Marks,
K-Level, CO</i> |
|--|-------------------------------|
| 1. State superposition theorem. | 2,K1,CO1 |
| 2. Define super node. | 2,K1,CO1 |
| 3. Draw the power triangle for AC circuits. | 2,K2,CO2 |
| 4. Which type of wire is used in house? | 2,K1,CO2 |
| 5. Give the essential parts of DC machine. | 2,K1,CO3 |
| 6. What are the two types of rotors of an induction motor? | 2,K1,CO3 |
| 7. Define the different operating regions of transistor. | 2,K1,CO4 |
| 8. List the types of DAC. | 2,K1,CO4 |
| 9. What is LVDT? | 2,K1,CO5 |
| 10. State the basic requirement of a measuring instrument. | 2,K1,CO5 |

PART - B (5 × 13 = 65 Marks)


Answer ALL Questions

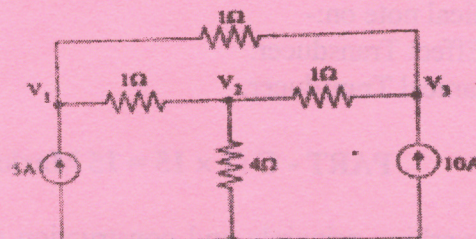11. a) By applying nodal method find the voltages V_1 , V_2 and V_3 for the given circuit. 13,K3,CO1



OR

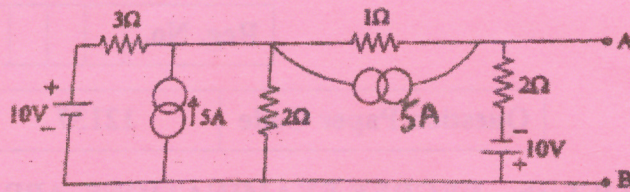- b) Draw the thevenin's equivalent circuit for the network between A and B. Also determine the thevenin's resistance & thevenin's voltage. 13,K2,CO1



12. a) An inductive coil of power factor 0.8 lagging is connected in series with a $120\mu\text{F}$ capacitor. When the series circuit is connected to a source to frequency 50Hz, it was observed that the magnitude of voltage across the coil and capacitor are equal. Determine the parameters of the coil. 13,K2,CO2

OR

- b) Illustrate the wiring materials and its accessories used for House wiring. 13,K2,CO2
13. a) (i) Derive the emf equation of the DC generator. 8,K2,CO3
(ii) Explain about DC separately excited DC generator. 5,K2,CO3

OR

- b) Explain the principle and construction of any two types of single phase induction motor. 13,K2,CO3
14. a) Illustrate the construction and working of PN diode and its characteristics with a neat sketch. 13,K2,CO4

OR

- b) Discuss about the following:-
(i) Weighted Resister type. 7,K2,CO4
(ii) R-2R type. 6,K2,CO4
15. a) With neat diagram explain about Linear Variable Differential Transformer and discuss its waveform. 13,K2,CO5

OR

- b) Write a technical note on:-
(i) Hall Effect Transducer. 7,K2,CO5
(ii) Mechanical Transducer. 6,K2,CO5

PART - C ($1 \times 15 = 15$ Marks)

16. a) Explain the working principle and construction of MI-Attraction and Repulsion type instrument. 15,K2,CO6

OR

- b) With a neat sketch explain about the working of Permanent Magnet Moving Coil (PMMC) and derive its torque equation. 15,K2,CO6