

M.E. / M.Tech. - DEGREE EXAMINATIONS, NOV/DEC 2022
 First Semester
M.E. - Embedded Systems Technologies
20PESPC101 - ADVANCED DIGITAL PRINCIPLES AND DESIGN
 (Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

- | | <i>Marks,</i> |
|--|--------------------|
| | <i>K-Level, CO</i> |
| 1. List the basic building blocks in ASM chart. | 2,K1,CO1 |
| 2. Distinguish between Moore and Mealy FSM. | 2,K2,CO1 |
| 3. Define implication table. | 2,K1,CO2 |
| 4. Define hazard in sequential circuits. | 2,K1,CO2 |
| 5. Define stuck at 1 fault. | 2,K1,CO3 |
| 6. Define essential test vector. | 2,K1,CO3 |
| 7. Define slave mode. | 2,K1,CO6 |
| 8. What are the applications of FPGA. | 2,K1,CO6 |
| 9. Write a VHDL code for JK FLIP FLOP using Behavioural model. | 2,K2,CO4 |
| 10. Write a VHDL code for NAND gate using a data flow model. | 2,K2,CO4 |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Design a sequence detector to detect the sequence 0111 using mealy and Moore FSM. 13,K2,CO1
- OR**
- b) Explain the design procedure for synchronous sequential circuits with an example. 13,K2,CO1
12. a) Show the reduced state table for a given state table using a merger diagram and implication table. 13,K2,CO2


Present state	next state		output	
	x=0	x=1	x=0	x=1
a	d	b	0	0
b	e	a	0	0

c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0


OR

- b) What are hazards? List its types. Explain in detail about the static 1 hazard with an example 13,K2,CO2

 13. a) (i) For the below circuit, determine the test vector which detects the stuck at 1 fault using path sensitization method. 5,K2,CO3



 - (ii) Analyze the given circuit using kohavi algorithm by a tests and b. test.



8,K2,CO3

OR

- b) Explain about fault diagnosis and testing process. 13,K2,CO3

14. a) Explain the design flow of FPGA. 13,K2,CO6

OR

- b) Explain the input, output blocks and programmable interconnects of Xilinx 4000 family. 13,K2,CO6

15. a) Write a VHDL code for ring counter. 13,K2,CO4

OR

- b) Write a VHDL code for half adder and full adder using a data flow model. 13,K2,CO4

PART - C (1 × 15 = 15 Marks)

16. a) Implement full adder and full subtractor using PAL

15,K2,CO5

OR

b) Implement BCD to excess 3 code convertor using PAL

15,K2,CO5