

06 FEB 2023

Reg. No.

COE

Question Paper Code

11682

B.E./B.Tech. - DEGREE EXAMINATIONS, NOV/DEC 2022

Third Semester

Electronics and Communication Engineering

20ECPC301 - DIGITAL ELECTRONICS

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

**PART-A (10 × 2 = 20 Marks)**

Answer ALL Questions

- |  | <i>Marks,<br/>K-Level, CO</i> |
|--|-------------------------------|
| 1. State De Morgan's theorem and mention its use.                  | 2, K1, CO1                    |
| 2. Convert binary 110111 into a decimal number system.             | 2, K2, CO1                    |
| 3. Draw the full adder circuit using half adder.                   | 2, K1, CO2                    |
| 4. Explain Combinational logic circuit?                            | 2, K2, CO2                    |
| 5. Explain how can race around conditions be eliminated?           | 2, K2, CO3                    |
| 6. Differentiate between the edge triggering and level triggering. | 2, K2, CO3                    |
| 7. State the rules for state reduction.                            | 2, K1, CO4                    |
| 8. Differentiate synchronous and asynchronous sequential circuits. | 2, K2, CO4                    |
| 9. Define noise margin.  | 2, K1, CO6                    |
| 10. Define power dissipation and propagation delay.                | 2, K1, CO6                    |

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) Use Quine Mccluskey method to simplify the given expression and verify your result using K-map  $F(A,B,C,D)=\sum(0,2,3,5,7,9,11,13,14)$ . 13, K3, CO1
- OR**
- b) Determine the minimum SOP expression  $F(A,B,C,D,E)=m(1,4,6,10,20,22,24,26)+d(0,11,16,27)$  using K-map method. Draw the circuit of the minimal expression using only NAND gates. 13, K3, CO1
12. a) With a neat diagram, explain in detail about the working of a 4-bit look ahead carry adder. Also mention its advantage over conventional adder. 13, K3, CO2
- OR**
- b) Construct a 4-bit comparator using logic gates. 13, K2, CO2

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

11682

13. a) Draw and explain the 4-bit SISO, SIPO, PISO and PIPO shift register with its waveforms. 13,K2,CO3

**OR**

- b) (i) Explain the operation of JK flip flop with neat diagram. 7,K2,CO3  
(ii) Convert to D flip-flop from a J-K flip-flop. 6,K2,CO3

14. a) Construct a MOD-10 synchronous counter using JK flip flops. Write an execution table and state table. 13,K3,CO4

**OR**

- b) Explain dynamic and essential hazard with an example. 13,K2,CO4

15. a) Construct the following four Boolean functions using PAL. 13,K3,CO6

$$F1(W,X,Y,Z) = \sum m(0,1,2,3,7,9,11)$$

$$F2(W,X,Y,Z) = \sum m(0,1,2,3,10,12,14)$$

$$F3(W,X,Y,Z) = \sum m(0,1,2,3,10,13,15)$$

$$F4(W,X,Y,Z) = \sum m(4,5,6,7,9,15)$$

**OR**

- b) Explain the operation of TTL with neat diagram. 13,K2,CO6

### PART C (1 × 15 = 15 Marks)

16. a) An asynchronous sequential circuit is described by the excitation and output functions. 15,K3,CO5

$$Y = x_1 x_2' + (x_1 + X_2')y$$

$$Z = Y$$

- (i) Draw the logic diagram of the circuit.  
(ii) Give the transition table and output map.  
(iii) Give the state flow table.

**OR**

- b) Construct an asynchronous sequential circuit with two inputs X and Y and with one output Z. Whenever Y is 1, input is transferred to Z. When Y is 0, the output does not change for any change in X. 15,K3,CO5