

Reg. No.

Question Paper Code

12077

24 JUL 2023

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2023

Fourth Semester

Electronics and Communication Engineering

20ECPW402 - LINEAR INTEGRATED CIRCUITS WITH LABORATORY

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

- | | <i>Marks,
K-Level, CO</i> |
|---|-------------------------------|
| 1. Mention the ideal DC characteristics of OP-amp. | 2,K2,CO1 |
| 2. Define slew rate. | 2,K1,CO1 |
| 3. Draw the circuit diagram of voltage follower using Op-amp. | 2,K2,CO2 |
| 4. Give the features of precision rectifier. | 2,K1,CO2 |
| 5. List the applications of PLL. | 2,K1,CO3 |
| 6. What are the modes of operation of IC 555 timer? | 2,K1,CO3 |
| 7. Distinguish between R-2R ladder and weighted resistor type DACs. | 2,K2,CO4 |
| 8. Define the term resolution in analog-to-digital converters. | 2,K1,CO4 |
| 9. Compare fixed voltage regulator with adjustable voltage regulator. | 2,K2,CO5 |
| 10. Draw the functional block diagram of switched mode capacitor filter ICMF10. | 2,K2,CO5 |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

- | | |
|--|-----------|
| 11. a) Explain the AC and DC performance characteristics of op-amp. | 13,K2,CO1 |
| OR | |
| b) Elaborate the functions of internal building blocks of op-amp with neat sketch. | 13,K2,CO1 |
| 12. a) Illustrate the operation of Logarithmic and Anti-logarithmic amplifiers using op-amp. | 13,K2,CO2 |
| OR | |
| b) Elaborate the operation of adder and subtractor with necessary expressions. | 13,K2,CO2 |
| 13. a) Draw and explain the working of analog multiplier ICs and discuss its applications. | 13,K2,CO3 |

OR

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

12077

- b) Explain how IC 555 Timer is working as an astable multivibrator with necessary diagram. 13,K2,CO3
14. a) Construct the R-2R ladder DAC and explain its working with circuit Schematic. 13,K2,CO4
- OR**
- b) Elucidate the working of successive approximation type ADC with neat sketch. 13,K2,CO4
15. a) Explain the principle of triangular wave generator circuit using op-amp and mention its applications. 13,K2,CO5
- OR**
- b) Explain RC phase shift oscillator using op-amp with suitable circuit diagram and derive the expression for frequency of oscillation. 13,K2,CO5

PART - C (1 × 15 = 15 Marks)

16. a) Design a monostable multivibrator using IC741 for a pulse period of 2 μ s. 15,K2,CO6
- OR**
- b) Explain Wien bridge oscillator and derive its frequency of oscillation. 15,K2,CO6