

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12465
---------------------	-------

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023

Second Semester

Computer Science and Business Systems

20BSPH205 - PRINCIPLES OF ELECTRONICS

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

- | | <i>Marks,
K-Level, CO</i> |
|---|-------------------------------|
| 1. What is doping and dopant? Give examples. | <i>2,K1,CO1</i> |
| 2. Why silicon semiconductor preferred than all other semiconductors? | <i>2,K1,CO1</i> |
| 3. Define clippers. | <i>2,K1,CO2</i> |
| 4. Sketch full wave bridge rectifier circuit. | <i>2,K2,CO2</i> |
| 5. Distinguish between PNP and NPN transistors. | <i>2,K2,CO3</i> |
| 6. Define stability factor. | <i>2,K1,CO3</i> |
| 7. What are the two advantages of negative feedback? | <i>2,K2,CO4</i> |
| 8. List out the Barkhausen criteria for oscillations. | <i>2,K1,CO4</i> |
| 9. What are the conditions for ideal operational amplifier? | <i>2,K1,CO5</i> |
| 10. What is flip flop? | <i>2,K1,CO5</i> |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

- | | |
|--|------------------|
| 11. a) (i) Explain Energy band in solid. | <i>8,K2,CO1</i> |
| (ii) Classify material on the basic forbidden energy gap. | <i>5,K2,CO1</i> |
| OR | |
| b) Explain Energy band diagram for P type and N type semiconductors. | <i>13,K2,CO1</i> |
| 12. a) What is PN junction diode? How PN junction are formed. Explain. | <i>13,K2,CO2</i> |
| OR | |
| b) What is Half wave rectifier? Explain the working of half wave rectifier circuit diagram and its parameters. | <i>13,K2,CO2</i> |
| 13. a) Explain an experiment to determine the characteristics of a transistor in CE configuration. Explain how transistor parameters can be evaluated. | <i>13,K3,CO3</i> |

OR

b) What is MOSFET? Explain construction and working of EMOSFET. *13,K2,CO3*

14. a) Derive an expression for voltage gain of an amplifier with negative feedback and positive feedback. *13,K2,CO4*

OR

b) Write down the various characteristics of topology. *13,K2,CO4*

15. a) Describe an operational amplifier. Explain its action as (i) Inverting amplifier (ii) Non inverting amplifier. *13,K2,CO5*

OR

b) What is Counter? Explain Asynchronous counter with its neat diagram. *13,K2,CO5*

PART - C (1 × 15 = 15 Marks)

16. a) (i) Explain half adder and Full adder circuit using IC 7400 series. *10,K2,CO6*
(ii) Explain the working function AND gate using discrete components. *5,K2,CO6*

OR

b) (i) With a neat sketch, explain the Half subtraction and Full subtraction. *10,K2,CO6*
(ii) Construct a logic circuit using NAND gates only for $Y = \overline{A} + \overline{BC}$. *5,K2,CO6*