

Reg. No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12810
---------------------	-------

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024

Second Semester

Computer Science and Business Systems

20BSPH205 - PRINCIPLES OF ELECTRONICS

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

	Marks	K-Level	CO
1. List out any four properties of semiconducting material.	2	K1	CO1
2. Differentiate between n-type and p-type semiconductor.	2	K2	CO1
3. Define Knee voltage of the diode.	2	K1	CO2
4. What is the difference between ordinary diode and zener diode?	2	K2	CO2
5. Distinguish between PNP and NPN transistors.	2	K2	CO3
6. What is cut off region for FET?	2	K2	CO3
7. What are the advantages of negative feedback?	2	K1	CO4
8. Define band width stability.	2	K1	CO4
9. What are input terminals of an operational amplifier?	2	K1	CO5
10. What is comparator in Op-amp?	2	K1	CO5

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Explain the concept of hole current and doping in a semiconductor with a note essential requirements of doping and its methods.	13	K2	CO1
OR			
b) With neat sketch classify conductors, semiconductors and insulators based on band theory of solids.	13	K2	CO1
12. a) Explain with neat sketch the V-I (volt-ampere) characteristic of a p-n junction diode.	13	K2	CO2
OR			
b) i) Explain in detail the working of a full wave rectifier and derive the expression for its efficiency.	6	K2	CO2
ii) Write a short note on zener breakdown and avalanche breakdown.	7	K2	CO2
13. a) Explain an experiment to determine the characteristics of a Field effect transistor in C-S configuration. Explain how transistor parameters can be evaluated.	13	K2	CO3

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

12810

OR

b) What is CB configuration? Explain an experiment to determine the characteristics of a transistor in CB configuration. 13 K2 CO3

14. a) Write down the various characteristics of feedback amplifier topology and also explain the input and output impedance. 13 K3 CO4

OR

b) What is oscillator? Mention its types and also explain Barkhausen criteria conditions. 13 K2 CO4

15. a) Describe an operational amplifier. Explain its action as (i) Inverting amplifier (ii) Non inverting amplifier. 13 K2 CO5

OR

b) With neat sketch, explain the Half adder and Full adder circuit and also explain Half subtraction and Full subtraction. 13 K2 CO5

PART - C (1 × 15 = 15 Marks)

16. a) What is flip flop? Explain any two flip flop and its truth table and its modification. 15 K2 CO6

OR

b) Explain AND, OR, NOT and EXOR gates. Write its truth table and draw the logic diagram. 15 K2 CO6