

Reg. No.

Question Paper Code

12527

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023

Second Semester

Electronics and Communication Engineering**20ECPC201 - CIRCUIT ANALYSIS**

(Regulations 2020)

Duration: 3 Hours


Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

*Marks,
K-Level, CO
2,K2,CO1*

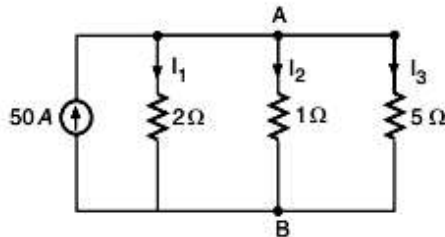1. Determine the current in all the resistors of the circuit given.




2. Define incidence matrix and tie-set matrix. *2,K1,CO1*
3. Relate the expression for Millman's equivalent source of n number of parallel connected voltage sources. *2,K2,CO3*
4. State maximum power transfer theorem. *2,K1,CO3*
5. Determine the quality factor of a coil for the series resonant circuit consisting of $R = 10 \Omega$, $L = 0.1\text{H}$, and $C = 10\mu\text{F}$. *2,K3,CO4*
6. Relate the expression for impedance of an RLC series circuit at half-power frequencies. *2,K1,CO4*
7. An RLC series circuit with $L = 2 \text{ H}$ and $C = 5 \text{ mF}$. Determine the value of R to give critical damping. *2,K2,CO5*
8. Define time constant of an RC circuit. *2,K1,CO5*
9. Give the condition for reciprocity and symmetrical condition for ABCD parameter. *2,K1,CO6*
10. State symmetrical properties of π networks. *2,K1,CO6*

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

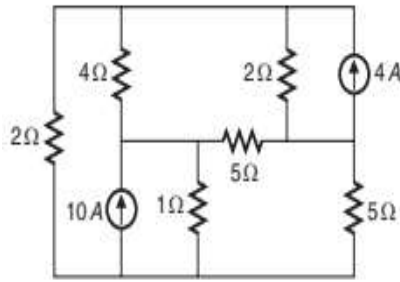
11. a) Determine the branch currents and voltages of the circuit given using a cut-set schedule. *13,K2,CO1*



OR


- b) Determine the cut-sets and cut-set matrix of the circuit shown in Fig.

13,K2,CO1

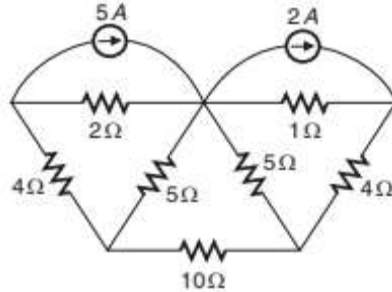

12. a) Determine the value of resistance that may be connected across terminals A and B so that maximum power is transferred from the circuit to the resistance. Also, estimate the maximum power transferred to the resistance.


13,K3,CO3

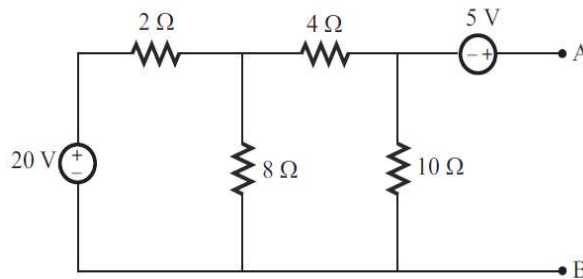

OR

- b) In the circuit of Fig. , use Millman's theorem to determine current through the 4Ω resistance.

13,K3,CO3

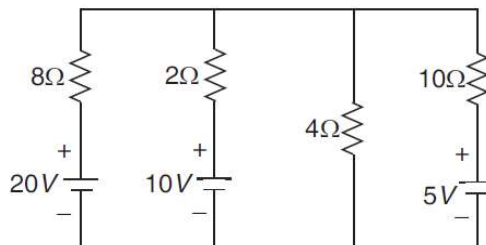

13. a) Consider two coils A and B consisting of 500 turns and 1500 turns, respectively. A current of 5 A in coil-A produces a flux of 0.6×10^{-3}

13,K3,CO4

Wb and the flux linking coil-B is 0.3×10^{-3} Wb. Determine the inductance, coefficient of coupling and mutual inductance of the coils.


OR

- b) A coil having an inductance of 100 mH is magnetically coupled to another coil having an inductance of 900 mH. The coefficient of coupling between the coils is 0.45. Calculate the equivalent inductance if the two coils are connected in a) series aiding, b) series opposing, c) parallel aiding and d) parallel opposing. 13,K3,CO4


14. a) An RL series circuit excited by a sinusoidal source $e(t) = 10 \sin 100t$ V by closing the switch at $t = 0$. Take $R = 10\Omega$ and $L = 0.1$ H. Determine the current $i(t)$ flowing through the RL circuit. 13,K2,CO5

OR

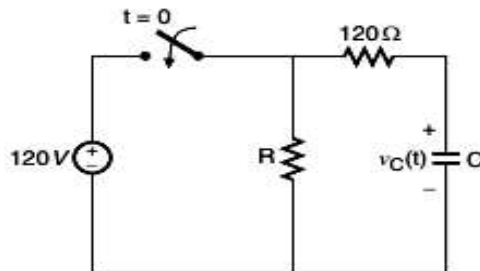- b) In the circuit of fig, the switch is open for a long time. On closing the switch at $t = 0$, the capacitor voltage rises to 70V in 10 ms. After the steady state is reached, the switch is opened again and found that the capacitor voltage is 90V in 0.5second. Find the value of R and C. 13,K2,CO5




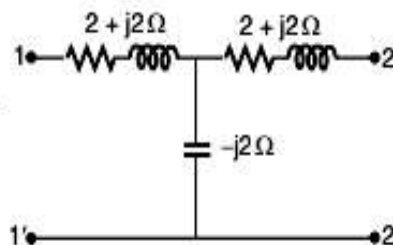15. a) Determine the admittance parameters of the T-network shown in Fig. 13,K2,CO6




OR

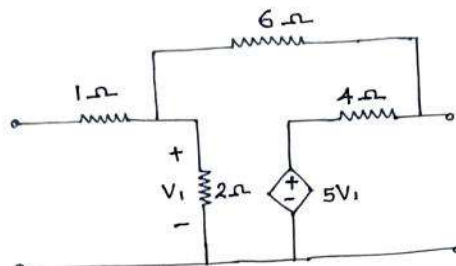- b) (i) Explain the method to find ABCD parameters of a 2 - port network. 5,K2,CO6
 (ii) Obtain the ABCD Parameters of the following two-port network. 8,K2,CO6



PART - C (1 × 15 = 15 Marks)

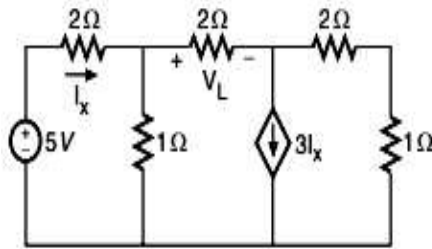16. a) Determine the voltage V_L in the circuit shown in Fig. 1, using mesh analysis. 15,K3,CO2



OR

- b) In the circuit shown in Fig, write mesh equations by inspection and solve V_x and I_x . Verify the result by node analysis. 15,K3,CO2

