

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12855
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024**

Third Semester

**Electronics and Communication Engineering**

**20ECPC301 – DIGITAL ELECTRONICS**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

	<i>Marks</i>	<i>K- Level</i>	<i>CO</i>
1. Give details about “maxterm” and “minterm”.	2	K2	CO1
2. Convert the given decimal number to their binary equivalent 108.364 and 268.025.	2	K2	CO1
3. Draw the full adder circuit using half adder.	2	K2	CO2
4. Define priority Encoder.	2	K1	CO2
5. Draw the state table and excitation table of the T flip flop.	2	K2	CO3
6. Differentiate between the edge triggering and level triggering.	2	K2	CO3
7. State the types of sequential circuits	2	K1	CO4
8. Define synchronous sequential circuit	2	K2	CO4
9. List the major differences between PLA and PAL	2	K2	CO6
10. Define power dissipation and propagation delay.	2	K1	CO6

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) Use Quine Mccluskey method to simplify the given expression and verify your result using K-map. F(A,B,C,D) = $\sum(0,2,3,5,7,9,11,13,14)$	13	K3	CO1
<b>OR</b>			
b) (i) Express the Boolean functions F=A+B’C in a sum of minterms.	6	K2	CO1
(ii) Express the following boolean expression in a simplified form using Boolean algebra.	7	K2	CO1
a) $x’y’z+x’yz+xy’$			
b) $xyz+x’z+yz$			
12. a) Construct a 4 bit BCD adder using full adder and explain its structure and compute the circuit to add 1001 and 0101. Write the sum and carry output of the given binary number.	13	K2	CO2

**OR**

- b) Construct a 4-bit comparator using logic gates. 13 K2 CO2
13. a) Explain the operation of master slave flip flop and show how the race around condition is eliminated. 13 K2 CO3
- OR**
- b) (i) Convert JK flip flop to T flip flop. 7 K2 CO3  
(ii) Explain the operation of D flip flop with neat diagram. 6 K2 CO3
14. a) Construct a MOD-10 synchronous counter using JK flip flops. Write an execution table and state table. 13 K2 CO4
- OR**
- b) Explain the different hazards in Combinational and sequential circuit. 13 K2 CO4
15. a) Use PLA to Implement the following functions. 13 K2 CO6  
 $A(x,y,z) = \sum m(1,2,4,6)$   
 $B(x,y,z) = \sum m(0,1,6,7)$   
 $C(x,y,z) = \sum m(2,6)$
- OR**
- b) Compare PROM, EPROM and EEPROM technologies. 13 K3 CO6

**PART - C (1× 15 = 15 Marks)**

16. a) An asynchronous sequential has two internal states and one output. The excitation and output functions describing the circuit are  
 $Y1 = X_1 X_2 + X_1 Y_2' + X_2' Y_1$   
 $Y2 = X_2 + X_1 Y_1' + Y_2 + X_1' Y_1$   
 $Z = X_2 + Y_1$   
 (i) Draw the logic diagram of the circuit  
 (ii) Give the transition table and output map  
 Give a flow table of the circuit. 15 K3 CO5
- OR**
- b) An asynchronous sequential circuit is described by the excitation and output functions.  
 $Y = X_1 X_2' + (X_1 + X_2')Y$   
 $Z = Y$   
 (i) Draw the logic diagram of the circuit  
 (ii) Give the transition table and output map  
 Give a flow table of the circuit 15 K3 CO5