

15. A bistable multivibrator has how many stable states? 1 K1 CO5
 (a) zero (b) one (c) two (d) either two or one
16. A bistable circuit with RC network in the negative-feedback becomes a...circuit 1 K1 CO5
 (a) Schmitt trigger (b) monostable (c) Astable (d) none of the mentioned
17. What is the main advantage of Class A power amplifiers despite their low efficiency? 1 K1 CO6
 (a) High efficiency in converting input power to output power
 (b) High linearity and low distortion
 (c) Low voltage gain
 (d) Low power handling capacity
18. In Class A power amplifiers, the transistor is biased in the region of its characteristics, which results in continuous conduction and constant power dissipation. 1 K1 CO6
 (a) Cutoff (b) Saturation (c) Linear (d) Active
19. A two-transistor class B amplifier is generally known as.... 1 K1 CO6
 (a) dual amplifier (b) symmetrical amplifier
 (c) differential amplifier (d) push pull amplifier
20. The transistor amplifier with 85% efficiency is likely to be a.... 1 K1 CO6
 (a) Class A amplifier (b) Class B amplifier (c) Class AB amplifier (d) Class C amplifier

PART - B (10 × 2 = 20 Marks)


Answer ALL Questions

21. Illustrate the function of Q-point. How it varies the output. 2 K2 CO1
22. Interpret the requirements of a biasing circuit. 2 K2 CO1
23. Define the voltage & current gain of an emitter follower. 2 K1 CO2
24. Draw the small signal equivalent circuit of the Common base amplifier using the h parameter model. 2 K1 CO2
25. State the Barkhausen Criterion for oscillation. 2 K1 CO3
26. List the topologies of a negative feedback amplifier. 2 K1 CO3
27. Infer the ideal response and actual response of tuned amplifiers with a diagram. 2 K2 CO4
28. Compare loaded Q and unloaded Q. 2 K2 CO4
29. Find the value of capacitors to be used in an astable multivibrator to provide a train of pulse 2 μsec wide at a repetition rate of 75 KHz with $R_1=R_2=10\text{ K}\Omega$. 2 K1 CO5
30. Classify Power amplifiers. 2 K2 CO6

PART - C (6 × 10 = 60 Marks)

Answer ALL Questions

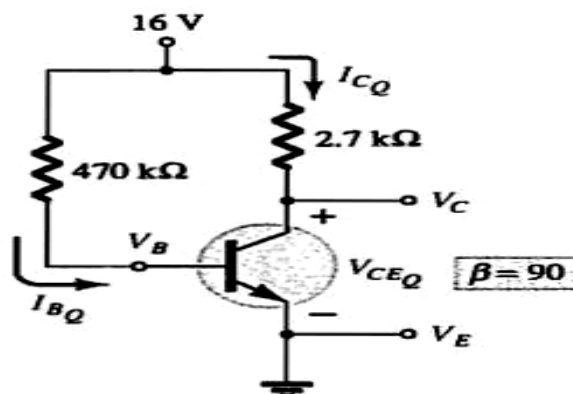31. a) For the fixed bias circuit Find the I_{BQ} , I_{CQ} , V_{CEQ} and V_C . 10 K2 CO1



OR

- b) Explain the stability factor S, S' and S'' of emitter bias circuit. 10 K2 CO1

32. a) Illustrate a CE amplifier & its small-signal equivalent. Derive its A_{vs} , A_i , R_{in} , R_o . 10 K2 CO2
OR
 b) Explain the principle of operation of a JFET amplifier. Derive Voltage gain, input and output impedance of common source JFET amplifiers with a neat circuit diagram of its small signal equivalent circuit. 10 K2 CO2
33. a) i) Illustrate the effects of negative feedback on the bandwidth of an amplifier. 5 K2 CO3
 ii) A negative feedback amplifier has voltage gain with feedback of 100. If the gain without feedback changes by 20% the gain with feedback should not vary more than 2%. Determine the value of the open loop gain and feedback ratio. 5 K2 CO3
OR
 b) Explain the working principle of RC phase shift oscillator circuit diagrams that also derive the expression for frequency of oscillation and condition for sustained oscillation. 10 K2 CO3
34. a) Show the double tuned amplifier with a neat circuit diagram and derive the expression for 3dB bandwidth. 10 K2 CO4
OR
 b) Illustrate the stability of tuned amplifiers and mention the need of neutralization. 10 K2 CO4
35. a) Illustrate the function of emitter coupled monostable Multivibrator and triggering methods for monostable multivibrator. 10 K2 CO5
OR
 b) Illustrate the triggering methods for a bistable multivibrator and explain it by necessary diagrams. 10 K2 CO5
36. a) Explain the working of Class B Push pull amplifiers with neat diagrams. Also derive its efficiency. 10 K2 CO6
OR
 b) Illustrate the transfer characteristic, signal waveforms, power dissipation, and power conversion efficiency of Class A amplifiers. 10 K2 CO6