

**B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2025**  
 Fourth Semester  
**Electronics and Communication Engineering**  
**20ECPW401 - ELECTRONIC CIRCUITS WITH LABORATORY**  
 Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (MCQ) (10 × 1 = 10 Marks)**

Answer ALL Questions

	<i>Marks</i>	<i>K- Level</i>	<i>CO</i>
1. Which of the following is used to determine the operating point of a transistor in a circuit? (a) AC load line      (b) DC load line      (c) Power curve      (d) Output curve	1	K1	CO1
2. Choose the following stability factors (S) is the best indicator of bias stability in a transistor circuit? (a) $S > 1$ (b) $S = 1$ (c) $S < 1$ (d) $S = 0$ Identify the amplifier configuration is most commonly used for impedance matching?	1	K1	CO1
3. (a) Common Emitter (CE)      (b) Common Base (CB) (c) Common Collector (CC)      (d) Differential Amplifier Infer the frequency response of an amplifier typically depends on:	1	K2	CO2
4. (a) The input impedance only (b) The output impedance only (c) The parasitic capacitances, inductances, and the circuit components (d) The power supply voltage Select the feedback configuration involves applying a feedback current in parallel with the	1	K1	CO3
5. input signal? (a) Voltage series feedback      (b) Voltage shunt feedback (c) Current series feedback      (d) Current shunt feedback	1	K1	CO3
6. The Barkhausen criterion for oscillations requires: (a) A phase shift of $90^\circ$ and a gain of 1 (b) A phase shift of $180^\circ$ and a gain of 1 or greater (c) A phase shift of $180^\circ$ and a gain of 2 (d) A phase shift of $360^\circ$ and a gain of 2	1	K1	CO4
7. What is the primary purpose of neutralization in tuned amplifiers? (a) To increase the gain of the amplifier (b) To cancel out the effects of parasitic capacitance (c) To stabilize the frequency response at high power (d) To reduce the input impedance of the amplifier Identify the multivibrator configuration is commonly used for frequency division and	1	K1	CO4
8. pulse generation? (a) Astable multivibrator      (b) Monostable multivibrator (c) Schmitt trigger      (d) Bistable multivibrator	1	K1	CO5
9. Identify the configuration of multivibrator is most suitable for switch debouncing? (a) Monostable      (b) Astable      (c) Bistable      (d) None of the above	1	K1	CO6
10. Which amplifier class minimizes crossover distortion? (a) Class A      (b) Class B      (c) Class AB      (d) Class C	1	K1	CO6

**PART - B (12 × 2 = 24 Marks)**

Answer ALL Questions

11. Define the operating point (Q-point) of a transistor.	2	K1	CO1
12. Show the purpose of emitter resistor in biasing.	2	K1	CO1
13. What is an AC load line?	2	K1	CO2

*K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create*

**14218**

- |   |   |    |     |
|---|---|----|-----|
| 14. Find CMRR of differential amplifier with differential gain 300 and common mode gain of 0.2.   | 2 | K1 | CO2 |
| 15. Recall negative feedback and its effect on amplifier performance.   | 2 | K1 | CO3 |
| 16. Identify the role of the tank circuit in tuned oscillator designs.  | 2 | K2 | CO3 |
| 17. How does cascading affect the bandwidth of tuned amplifiers?  | 2 | K1 | CO4 |
| 18. What is neutralization in amplifiers?   | 2 | K1 | CO4 |
| 19. A monostable multivibrator has an $R = 100 \text{ k}\Omega$ and $C = 0.01 \text{ }\mu\text{F}$ . Calculate the pulse width of the output. | 2 | K2 | CO5 |
| 20. What is hysteresis in a Schmitt Trigger?  | 2 | K1 | CO5 |
| 21. Infer crossover distortion in push-pull amplifiers.   | 2 | K2 | CO6 |
| 22. How does Class C amplifier achieve high efficiency?   | 2 | K1 | CO6 |

**PART - C (6 × 11 = 66 Marks)**

Answer ALL Questions

- |   |    |    |     |
|---|----|----|-----|
| 23. a) Infer voltage divider bias configuration. Draw the circuit diagram and derive the expression for collector current and stability factor.                             | 11 | K2 | CO1 |
| <b>OR</b>   |    |    |     |
| b) Outline the term bias stabilization and explain the concept of thermal runaway and methods to prevent it.  | 11 | K2 | CO1 |
| 24. a) Explain the basic common emitter amplifier circuit and derive the expressions for its small signal voltage gain, current gain, input impedance and output impedance. | 11 | K2 | CO2 |
| <b>OR</b>   |    |    |     |
| b) Explain the operation of cascade amplifier and derive voltage gain, overall input resistance, overall current gain and output impedance.                                 | 11 | K2 | CO2 |
| 25. a) Compare and explain the four basic feedback topologies: Voltage series, Voltage shunt, Current series, and Current shunt, with suitable examples.                    | 11 | K2 | CO3 |
| <b>OR</b>   |    |    |     |
| b) Draw the Circuit diagram of Wien Bridge oscillator and derive the expression for the frequency of Oscillations.  | 11 | K2 | CO3 |
| 26. a) Illustrate the frequency response of a double tuned amplifier. Explain how mutual inductance affects bandwidth.  | 11 | K2 | CO4 |
| <b>OR</b>   |    |    |     |
| b) Apply the concept of stagger tuning. How does it help in improving the bandwidth of tuned amplifiers?  | 11 | K2 | CO4 |
| 27. a) Illustrate the advantages of neutralization in high-frequency amplifiers? Explain with examples.   | 11 | K2 | CO5 |
| <b>OR</b>   |    |    |     |
| b) Illustrate the function of emitter coupled monostable Multivibrator and triggering methods for monostable multivibrator.   | 11 | K2 | CO5 |
| 28. a) Show the single-ended power amplifier and derive expressions for output power and power dissipation.   | 11 | K2 | CO6 |
| <b>OR</b>   |    |    |     |
| b) Illustrate the function of complementary symmetry push-pull amplifier circuit and its operation in detail.   | 11 | K2 | CO6 |