

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12508
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023**  
Fourth Semester  
**Electronics and Communication Engineering**  
**20ECPW402 - LINEAR INTEGRATED CIRCUITS WITH LABORATORY**  
(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

- |  | <i>Marks,<br/>K-Level, CO</i> |
|--|-------------------------------|
| 1. Define CMRR.  | 2,K1,CO1                      |
| 2. Define Slew rate and what causes slew rate.                             | 2,K1,CO1                      |
| 3. Illustrate the circuit of a Antilog amplifier.                          | 2,K2,CO2                      |
| 4. List the applications of comparator.                                    | 2,K1,CO2                      |
| 5. Visualize the basic building blocks of PLL.                             | 2,K1,CO3                      |
| 6. Illustrate the circuit of AM detector using PLL.                        | 2,K2,CO3                      |
| 7. Find the number of comparators required for realizing a 4bit flash ADC. | 2,K1,CO4                      |
| 8. List the main advantages of integrating type ADCs.                      | 2,K1,CO4                      |
| 9. List the various applications of multi vibrator.                        | 2,K1,CO5                      |
| 10. Define linear voltage regulator.                                       | 2,K1,CO5                      |

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) Explain the DC characteristics of the operational amplifier. 13,K2,CO1
- OR**
- b) List and explain the function of all the basic building blocks of an operational amplifier. 13,K2,CO1
12. a) With neat sketch explain the operation of an instrumentation amplifier. 13,K2,CO2
- OR**
- b) Derive the gain of inverting and non-inverting amplifier. 13,K2,CO2
13. a) Explain briefly about application of analog multiplier ICs. 13,K2,CO3
- OR**

- b) Discuss the following applications of Analog Multiplier ICs *13,K2,CO3*  
(i) Voltage squarer.  
(ii) Voltage divider.  
(iii) Square rooter.  
(iv) Phase angle detector.

14. a) Explain the following Digital to Analog & Analog to Digital conversion techniques. *13,K2,CO4*  
(i) Flash type ADC.  
(ii) Weighted resistor DAC.

**OR**

- b) Draw and explain the sample and hold circuit. *13,K2,CO4*

15. a) Explain the working principle and salient features of RC phase shift oscillator using IC741. *13,K2,CO5*

**OR**

- b) Differentiate between the low pass, high pass and band pass filter. *13,K2,CO5*  
Sketch the frequency plot.

**PART - C (1 × 15 = 15 Marks)**

16. a) Draw and explain the regenerative comparator circuit and obtain expression for  $V_{UT}$  and  $V_{LT}$ . *15,K2,CO6*

**OR**

- b) Design an Integrator for a frequency of operation of 1KHz. *15,K2,CO6*