

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	14227
---------------------	-------

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2025

Fourth Semester

Electronics and Communication Engineering

20ECPW402 - LINEAR INTEGRATED CIRCUITS WITH LABORATORY

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (MCQ) (10 × 1 = 10 Marks)

Answer ALL Questions

	Marks	K- Level	CO
1. Slew rate is defined as the rate of change of _____.	1	K1	CO1
(a) Output voltage with respect to time			
(b) Input voltage with respect to time			
(c) Both output input voltage with respect to time			
(d) None of the mentioned			
2. Which of the following electrical characteristics is not exhibited by an ideal op-amp?	1	K1	CO1
(a) Infinite voltage gain			
(b) Infinite bandwidth			
(c) Infinite output resistance			
(d) Infinite slew rate			
3. The circuit in which the output voltage waveform is the integral of the input voltage waveform is called _____.	1	K1	CO2
(a) Integrator			
(b) Differentiator			
(c) Phase shift oscillator			
(d) Square wave generator			
4. Which application use differentiator circuit?	1	K1	CO2
(a) None of the mentioned			
(b) FM modulators			
(c) Wave generators			
(d) Frequency Shift keying			
5. Choose the op-amp that improves the filter performance.	1	K1	CO3
(a) μ A741			
(b) LM318			
(c) LM101A			
(d) MC34001			
6. Which circuit can be used to take square root of a signal?	1	K1	CO3
(a) Divider circuit			
(b) Multiplier circuit			
(c) Squarer circuit			
(d) None of the mentioned			
7. At which state the phase-locked loop tracks any change in input frequency?	1	K1	CO4
(a) Free running state			
(b) Capture state			
(c) Phase locked state			
(d) All of the mentioned			
8. The practical use of binary-weighted digital-to-analog converters is limited to _____.	1	K1	CO4
(a) 4-bit D/A converter			
(b) 8-bit D/A converter			
(c) R-2R Ladder D/A converter			
(d) op-amp comparator			
9. How many control lines are present in analog to digital converter in addition to reference voltage?	1	K1	CO4
(a) Three			
(b) Two			
(c) One			
(d) None of the mentioned			
10. Which filter type is called a flat-flat filter?	1	K1	CO6
(a) Cauer filter			
(b) Butterworth filter			
(c) Chebyshev filter			
(d) Band-reject filter			

PART - B (12 × 2 = 24 Marks)

Answer ALL Questions

11. Why is the slew rate infinite in ideal op-amp?	2	K1	CO1
12. Find the maximum frequency for a sine wave output voltage of 12v peak with an OP-AMP whose slew rate is 0.5V/ μ s.	2	K2	CO1
13. What is the function of a phase shift circuit?	2	K1	CO2
14. How are the current characteristics of PN junction employed in log amplifier?	2	K1	CO2
15. Define Capture range, Lock in range, Pull in time.	2	K1	CO3
16. List the basic building block of a PLL.	2	K1	CO3
17. What are the drawbacks of binary weighted resistor D/A converter?	2	K1	CO4
18. Define settling time.	2	K1	CO4

- | | | | | |
|-----|--|---|----|-----|
| 19. | What is the necessity of having input and output capacitors in three terminal IC regulators? | 2 | K1 | CO5 |
| 20. | List the various application of Multivibrator | 2 | K1 | CO5 |
| 21. | What are an isolation amplifier and its application's? | 2 | K1 | CO6 |
| 22. | List the advantage of a switched capacitor filter. | 2 | K1 | CO6 |

PART - C (6 × 11 = 66 Marks)

Answer ALL Questions

- | | | | | |
|-----------|---|----|----|-----|
| 23. | a) Explain about Ideal Op-Amp with suitable diagrams. | 11 | K2 | CO1 |
| OR | | | | |
| | b) Draw the transfer characteristics of an operational amplifier and explain the linear and non-linear operation. | 11 | K2 | CO1 |
| 24. | a) (i) Explain the operation of precision full wave rectifier with neat sketch. | 7 | K2 | CO2 |
| | (ii) Illustrate the working of voltage to current converter. | 4 | K2 | CO2 |
| OR | | | | |
| | b) Interpret the circuit that performs the mathematical operation of differentiation. Draw its output waveform. | 11 | K2 | CO2 |
| 25. | a) Illustrate the working of analog multiplier using emitter coupled transistor pair. | 11 | K2 | CO3 |
| OR | | | | |
| | b) Explain the application of PLL as AM Detector and FSK Demodulator. | 11 | K2 | CO3 |
| 26. | a) Explain in detail on the operational features of 4 – bit weighted resistor type D/A converter. | 11 | K2 | CO4 |
| OR | | | | |
| | b) With neat sketch explain the working of a flash type ADC. | 11 | K2 | CO4 |
| 27. | a) Compare the working of astable and monostable multi vibrator using IC555 timer. | 11 | K2 | CO5 |
| OR | | | | |
| | b) Explain the working principle of Triangular wave generator circuit using op-amp and mention its application. | 11 | K2 | CO5 |
| 28. | a) With a neat circuit diagram, explain the working of linear voltage regulator using operational amplifier. | 11 | K2 | CO6 |
| OR | | | | |
| | b) Explain the following ICs function and application of Audio Power Amplifier. | 11 | K2 | CO6 |