

Reg. No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12715
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024**

Fourth Semester

**Electronics and Communication Engineering**

**20ECPW402 - LINEAR INTEGRATED CIRCUITS WITH LABORATORY**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

	Marks	K- Level	CO
1. List the ideal characteristics of an operational amplifier.	2	K1	CO1
2. A 100pF capacitor has a maximum charging current of 100 micro amps. Find its slew rate.	2	K1	CO1
3. Show that the peak detector is capable of holding the peak value.	2	K1	CO2
4. Describe Hysteresis. Mention the causes of Hysteresis in comparator.	2	K1	CO2
5. Mention the purpose of having a low pass filter in PLL.	2	K1	CO3
6. List the applications of 555 Timer IC.	2	K1	CO3
7. List the specifications of ADC and DAC.	2	K1	CO4
8. An 8 bit A/D converter accepts an input voltage signal of range 0 to 12v. What is the digital output for an input voltage of 6V?	2	K2	CO4
9. Define Line and Load regulation.	2	K1	CO5
10. State the uses of switched capacitor filters.	2	K1	CO5

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) Describe the AC and DC Characteristics of op amp.	13	K2	CO1
<b>OR</b>			
b) Write a note on stability criteria and frequency compensation Technique applied in op-amp.	13	K2	CO1
12. a) With a neat diagram explain the application of op amp as a Clipper and Clamper.	13	K2	CO2
<b>OR</b>			
b) Define precision rectifier? With circuit schematic explain the working principle of Half wave and full wave rectifier.	13	K2	CO2
13. a) Describe the functional block diagram of PLL and explain all the major components of PLL with equations.	13	K2	CO3

**OR**

- b) i) Discuss any two applications of Analog Multiplier ICs. 5 K2 CO3  
ii) Draw and explain the operation of VCO IC 566. 8 K2 CO3
14. a) i) Explain the working of R-2R ladder type DAC. 8 K2 CO4  
ii) Draw and explain the sample and hold circuit. 5 K2 CO4

**OR**

- b) i) Explain the operation of Flash type ADC. 8 K2 CO4  
ii) Discuss the specifications of data convertors. 5 K2 CO4
15. a) Explain the operation of a monolithic switching regulator. 13 K2 CO5

**OR**

- b) Trace and explain the functional diagram of IC723 General purpose voltage regulator. 13 K2 CO5

**PART - C (1 × 15 = 15 Marks)**

16. a) Design and describe a Monostable multivibrator using IC741 for a pulse period of 2  $\mu$ s. 15 K3 CO6

**OR**

- b) i) Describe a RC phase shift oscillator with the sustained oscillation for  $|A| \geq 29$ . 8 K3 CO6  
ii) Design an RC phase shift oscillator to oscillate at 100Hz. Assume  $R=6.5K\Omega, C=0.1\mu F$ . 7 K3 CO6