

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12528
---------------------	-------

B.E. / B.Tech - DEGREE EXAMINATIONS, NOV / DEC 2023

Second Semester

Electrical and Electronics Engineering

(Common Electronics and Instrumentation Engineering & Instrumentation and control Engineering)

20EEPC201 - ELECTRICAL CIRCUIT ANALYSIS

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)


Answer ALL Questions

- | | |
|---|--------------------|
| | <i>Marks,</i> |
| | <i>K-Level, CO</i> |
| 1. Estimate the resultant resistance produced by the parallel connection of two resistors of 10Ω and 30Ω. | 2,K2,CO1 |
| 2. How the series circuit is distinguished with parallel circuits? | 2,K2,CO1 |
| 3. State maximum power transfer theorem for DC circuits. | 2,K1,CO2 |
| 4. State Reciprocity theorem. | 2,K1,CO2 |
| 5. A series RC circuit consists of a resistor 10Ω and capacitor of 0.1F. Find the time constant τ. | 2,K2,CO3 |
| 6. What is meant by transient time? | 2,K1,CO3 |
| 7. Express the term tuned circuits. Mention the different of tuned circuits. | 2,K1,CO4 |
| 8. Write the expression for resonant frequency for Parallel RLC Circuit. | 2,K1,CO4 |
| 9. Compare star and delta connected system. | 2,K2,CO5 |
| 10. Define power factor in terms of impedance and power components. | 2,K1,CO5 |

PART - B (5 × 13 = 65 Marks)


Answer ALL Questions

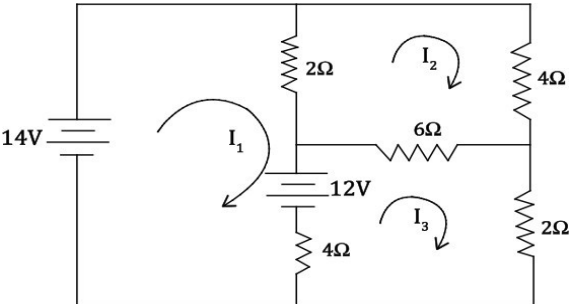11. a) Illustrate the Loop currents I_1 , I_2 and I_3 by Mesh loop analysis as shown in Fig. 13,K3,CO1




OR

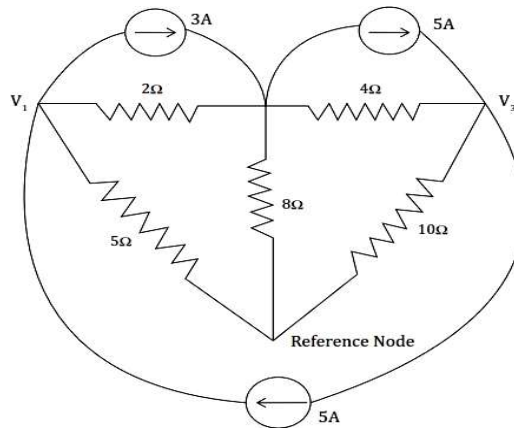- b) Calculate the value of Nodal Voltages V_1 , V_2 and V_3 by nodal analysis method as shown in Fig. 13,K3,CO1




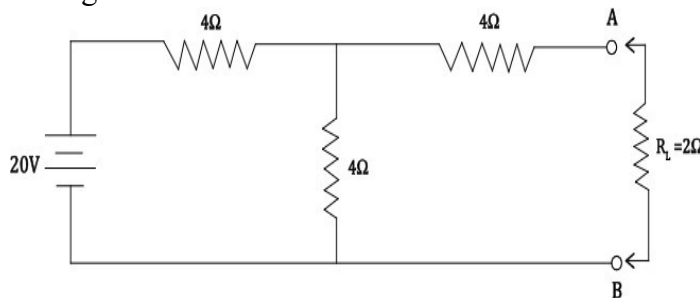12. a) Prove Thevenin's theorem and Norton's theorem for the given problem as shown in Fig. 13,K3,CO2



OR

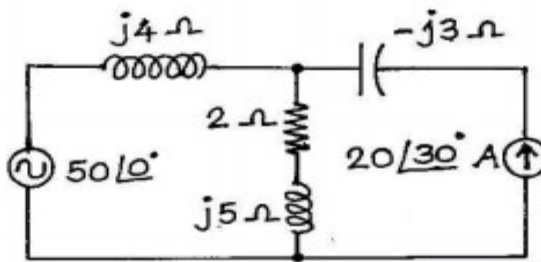- b) For the circuit shown below, determine the voltage across $(2+j5)\Omega$ impedance by using the superposition theorem. 13,K3,CO2




13. a) Derive the transient response of series R-L circuit, with DC input, using Laplace transform and also sketch the transient response curve. 13,K2,CO3

OR

- b) A Series RLC circuit with $R=20\ \Omega$, $L=0.05\ \text{H}$ and $C=20\ \mu\text{F}$ has a constant voltage $V=100\ \text{V}$ applied at $t=0$. Determine the current transient. 13,K3,CO3

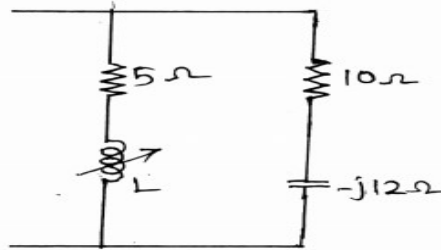14. a) Analyze the value of L at which the circuit resonates at a frequency of 1000 rad/s in the circuit shown in Fig. 13,K3,CO4



OR

- b) Explain the phenomenon of resonance. Derive the formula for the resonance frequency of the series resonance circuits. And also obtain the Capacitance and resonance curve. 13,K2,CO4
15. a) A 400V , three phase supply feeds an un balanced, Delta connected load. The branch impedances of the load are $Z_R=(4+j8)\Omega$; $Z_Y=(3+j4)\Omega$ and $Z_B=(15+j20)\Omega$. Find the line currents and Power across each phase. Assume RYB phase sequence. 13,K3,CO5

OR

- b) Explain three phase power measurement by 2 wattmeter method for star connected load and determine the power equation and draw the phasor diagram. 13,K2,CO5

PART - C (1 × 15 = 15 Marks)

16. a) (i) A three phase balanced delta-connected load of $4+j8\Omega/\text{Phase}$ is connected across a 400V , 3ϕ balanced supply. Determine the phase currents and Power (Phase sequence in RYB). 10,K3,CO5
- (ii) Explain in detail in the Concept of co-efficient coupling. 5,K2,CO4

OR

- b) (i) A balanced Star connected load of $(4+j3) \text{ Ohm / Phase}$ is connected to a 3-Phase, 230V , 50Hz Supply. Evaluate (i) Line Current (ii) Power Factor (iii) Power. 10,K3,CO5
- (ii) Two coupled coils of self inductance $L_1 = 2\text{H}$ and $L_2 = 4 \text{ H}$ are coupled in (i) series aiding (ii) series opposing (iii) parallel aiding (iv) parallel opposing. If the mutual inductance is 0.5H . Find the equivalent inductance in each case. 5,K2,CO4