

Reg. No.

Question Paper Code

12652

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024

Second Semester

Electrical and Electronics Engineering

(Common to Electronics and Instrumentation Engineering & Instrumentation and Control Engineering)

20EEPC201 - ELECTRICAL CIRCUIT ANALYSIS

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)


Answer ALL Questions

- | | <i>Marks</i> | <i>K-
Level</i> | <i>CO</i> |
|--|--------------|---------------------|-----------|
| 1. Define Ohm's law with its limitations. | 2 | K1 | CO1 |
| 2. List the importance of power factor. | 2 | K1 | CO1 |
| 3. Justify the condition for maximum power transfer theorem. | 2 | K2 | CO2 |
| 4. List out the procedure to calculate Norton's Current. | 2 | K2 | CO2 |
| 5. Define the time constant for RL circuit. | 2 | K1 | CO3 |
| 6. Compare between the steady state and the transient response of an electrical circuit. | 2 | K2 | CO3 |
| 7. Define quality factor of series resonance circuit. | 2 | K1 | CO4 |
| 8. Show the equation of coefficient of coupling. | 2 | K2 | CO4 |
| 9. What is real power and reactive power of AC circuits? | 2 | K2 | CO5 |
| 10. Show the relation between Line current and Phase current for Star and Delta Network. | 2 | K2 | CO5 |


PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

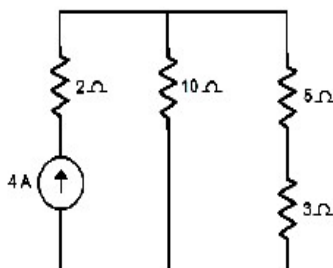11. a) i) Show the current through 10 Ω resistor for the following circuit. 6 K2 CO1




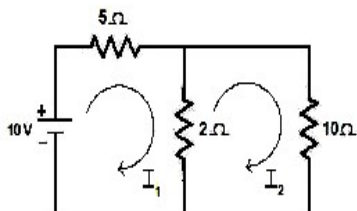- ii) Explain the mesh equations for the circuit shown in figure below and solve the currents. 7 K2 CO1




OR

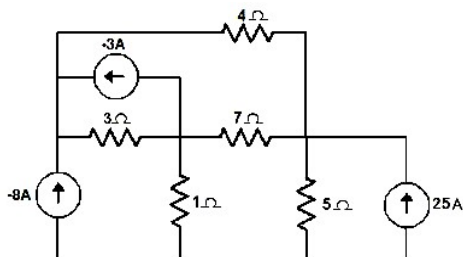- b) Infer the nodal voltages for the given circuit and also obtain the power dissipation across 5Ω resistor. 13 K2 CO1




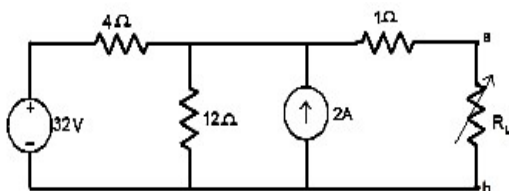12. a) Identify the Thevenin's equivalent circuit of the circuit shown below, to left of the terminals ab. Then find the current through $R_L = 16\Omega$ and 36Ω . 13 K3 CO2



OR

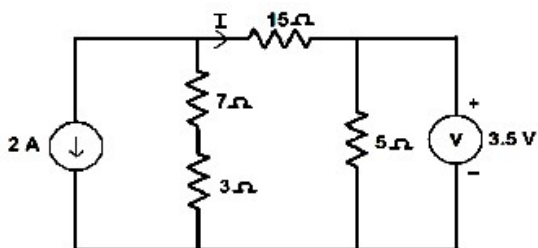- b) Solve for the circuit shown by using superposition theorem to compute current (I). 13 K3 CO2



13. a) A Series RLC circuit has $R=50\Omega$, $L=0.2H$, and $C=50$ microfarad. Constant voltage of $100V$ is impressed upon the circuit at $t=0$. Find the expression for the transient current assuming initially relaxed conditions. 13 K2 CO3

OR

- b) A step voltage $V(t) = 100 u(t)$ is applied to a series RLC circuit with $L=10H$, $R=2\Omega$ and $C=5F$. The initial current in the circuit is zero but there is an initial voltage of $50V$ on the capacitor in a direction which opposes the applied source. Find the expression for the current in the circuit. 13 K2 CO3

14. a) Derive bandwidth for a series RLC circuit as a function of resonant frequency. 13 K2 CO4

OR

- b) A series RLC circuit consists of $R=100\ \Omega$, $L = 0.02\ \text{H}$ and $C = 0.02\ \mu\text{F}$. Calculate frequency of resonance. A variable frequency sinusoidal voltage of constant RMS value of 50V is applied to the circuit. Find the frequency, when the voltage across L and C is maximum. Also calculate the maximum voltage across L and C. Also calculate voltages across L and C at frequency of resonance. Find maximum current in the circuit. 13 K2 CO4
15. a) A symmetrical three phase 400V system supplies a balanced delta connected load. The current in each branch circuit is 20A and phase angle 40° (lag) calculate the line current and total power. 13 K2 CO5
- OR**
- b) A balanced star connected load having an impedance $15+j20\ \Omega$ per phase is connected to $3\ \emptyset$, 440V, 50Hz. Find the line current and power absorbed by the load. 13 K2 CO5

PART - C (1× 15 = 15 Marks)

16. a) Outline the single tuned circuit and derive the expression for mutual inductance and current in the secondary coil. 15 K2 CO4
- OR**
- b) With a neat circuit and phasor diagram explain the three-phase power measurement by two wattmeter method. 15 K2 CO5