

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12856
---------------------	-------

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024

Third Semester

Electrical and Electronics Engineering
20EPC301 - ANALOG ELECTRONICS

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)


Answer ALL Questions

- | | Marks | K-
Level | CO |
|---|-------|-------------|-----|
| 1. Define thermal runaway in IGBT. | 2 | K1 | CO1 |
| 2. Why IGBT is popular in recent days? | 2 | K1 | CO1 |
| 3. How power amplifiers are classified? | 2 | K1 | CO2 |
| 4. List the advantages and disadvantages of a phase shift oscillator. | 2 | K | CO2 |
| 5. Mention the characteristics of an ideal op-amp. | 2 | K1 | CO3 |
| 6. Define slew rate. What is its significance? | 2 | K1 | CO3 |
| 7. List the features of instrumentation amplifier. | 2 | K1 | CO4 |
| 8. Which is the fastest ADC and why? | 2 | K2 | CO4 |
| 9. Draw the pin diagram of IC 555 timer. | 2 | K1 | CO5 |
| 10. How current boosting is achieved in IC723? | 2 | K2 | CO5 |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

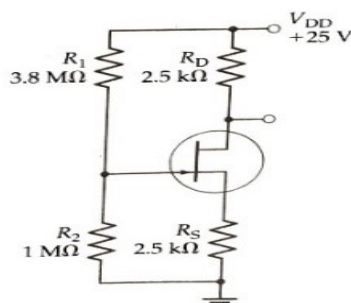11. a) Determine $I_{D(\min)}$, $I_{D(\max)}$, $V_{DS(\min)}$, $V_{DS(\max)}$ for the voltage divider bias circuit shown in the figure. 13 K2 CO1



OR

- b) Explain the DC and AC load line analysis of BJT. 13 K2 CO1
12. a) Describe the working of class A and class B power amplifier in detail with relevant diagram. 13 K2 CO2

OR

b) Explain the operation of wein bridge oscillator with neat diagram. 13 K2 CO2

13. a) Explain the following terms in an op-amp 13 K2 CO3
(i) Bias current.
(ii) Thermal drift.
(iii) Input offset voltage and current.
(iv) Virtual ground.

OR

b) Explain the application of op-amp as differentiator and integrator. 13 K2 CO3

14. a) Draw the circuit of monostable multivibrator and obtain the expression. 13 K2 CO4

OR

b) Explain the principle of operation of successive Approximation ADC. 13 K2 CO4

15. a) Draw and explain the functional block diagram of 723 regulators. 13 K2 CO5

OR


b) Draw the block diagram of the function generator ICL 8038 and explain its operation. 13 K2 CO5

PART - C (1 × 15 = 15 Marks)

16. a) i) Explain the principle of operation of crystal oscillator with neat diagram. 9 K5 CO2
ii) In an RC phase shift oscillator if $R_1=R_2=R_3= 200k\Omega$ and $C_1=C_2=C_3= 100Pf$ estimate the frequency of oscillation. 6 K5 CO2

OR

b) 15 K5 CO3

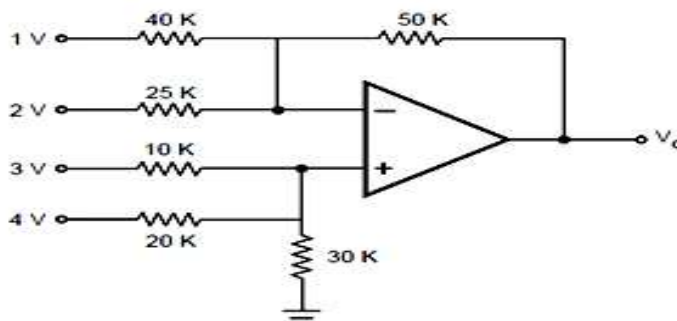

Determine the output voltage for the circuit.