

Reg. No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12915
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024**

Third Semester

**Electrical and Electronics Engineering**  
**20EEPC304 - DIGITAL LOGIC CIRCUITS**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

	Marks	K- Level	CO
1. Design AND gate using only NAND gates.	2	K2	CO1
2. Apply De-Morgan's theorem to simplify $(A'+BC)'$ .	2	K2	CO1
3. Write the Standard canonical POS form of $F=A.(A+B)'$ .	2	K2	CO2
4. List the applications of Multiplexer.	2	K1	CO2
5. Differentiate latch and flip flop.	2	K2	CO3
6. Give characteristic equation for D and T flip flops.	2	K2	CO3
7. Explain Dynamic Hazard.	2	K1	CO4
8. Define critical race.	2	K1	CO4
9. Draw the general architecture of CPLD.	2	K1	CO5
10. Explain the declaration of entity in VHDL.	2	K1	CO5

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) Explain the operation of DTL with suitable example.	13	K2	CO1
--	----	----	-----

**OR**

b) i) Find the hexadecimal equivalent of the decimal number 256 and the octal equivalent of the decimal number 64.	6	K3	CO1
ii) Assume that the code word 1001100 is transmitted and that 1000100 is received. The receiver does not know what was transmitted and must look for proper parities to determine if the code is correct. Designate any error that has occurred in transmission if even parity is used.	7	K3	CO1
12. a) i) Implement the following Boolean functions, using Suitable Multiplexer: $F(w, x, y, z) = \sum (2, 3, 10, 11, 12, 13, 14, 15)$	6	K3	CO2
ii) Design and explain the operation of Half adder.	7	K4	CO2

**OR**

- b) i) Design and Explain the operation of Binary to excess-3 code convertor. 6 K4 CO2  
 ii) Implement full adder using DEMUX. 7 K3 CO2

13. a) Demonstrate 3 bit Asynchronous down counter using JK flipflop. 13 K2 CO3

**OR**

- b) Design a combinational circuit with three inputs, x, y and z, and the three outputs, A, B, and C. When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary' input is 4, 5, 6, or 7, the binary output is one less than the input. 13 K4 CO3

14. a) Design hazard free circuit for the following: 13 K4 CO4  
 $F(A,B,C,D)=\sum(2,5,6,7,10,13,15)$


**OR**

- b) Design a pulse mode circuit with inputs x1,x2. one output z. The circuit should produce an output pulse to coincide with the last input pulse in the sequence x1-x2-x2. No other input sequence should produce an output pulse. Use T flipflops. 13 K4 CO4

15. a) Build a VHDL code to realize full adder in dataflow modelling, behavioural and structural modelling. 13 K3 CO5

**OR**

 - b) Develop VHDL code for the circuit shown: 13 K4 CO5



**PART - C (1 × 15 = 15 Marks)**

16. a) i) Implement the following using PAL:- 8 K3 CO5  
 $A=\sum m(1,2,4,6)$  ;  $B=\sum m(0,1,3,6,7)$   
 $C=\sum m(1,2,4,6,7)$  ;  $D=\sum m(1,2,3,5,7)$   
 ii) Minimize using K-Map:  $F(A, B, C, D) = \sum (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$  7 K3 CO2

**OR**

- b) i) Convert the following: 8 K3 CO1  
 $(56)_{10} = (\underline{\quad} ? \underline{\quad})_8$   
 $(223)_{10} = (\underline{\quad} ? \underline{\quad})_{16}$   
 ii) An asynchronous sequential circuit is described by the following excitation and output function,  $Y=x_1 x_2 +(x_1+x_2)y$   $Z= y$  Predict the logic diagram of the circuit, Interpret the transition table and the output map, Obtain its flow table. 7 K3 CO4