

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12846
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024**

Fifth Semester

**Electrical and Electronics Engineering**  
**20EEPC501 - POWER SYSTEM ANALYSIS**

Regulations - 2020

**Duration: 3 Hours**

**Max. Marks: 100**

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

	<i>Marks</i>	<i>K- Level</i>	<i>CO</i>
1. What is a single line diagram?	2	K1	CO1
2. State the advantages of per unit computation.	2	K1	CO1
3. What is the need for load flow study?	2	K2	CO2
4. Compare Gauss-Seidal and Newton Raphson method of load flow analysis.	2	K2	CO2
5. What are the causes for a balanced fault in a power system?	2	K1	CO3
6. What is sub transient reactance?	2	K1	CO3
7. Find the positive sequence current, if $I_a=18\angle 0^\circ$ A, $I_b= 10\angle -30^\circ$ A, and $I_c=10\angle 30^\circ$ A.	2	K1	CO4
8. Draw the zero sequence networks for a Star-Delta transformer.	2	K2	CO4
9. What is a power angle curve?	2	K1	CO5
10. Define critical clearing angle and critical clearing time.	2	K2	CO5

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) Determine Y bus for the 3 bus system. The line series impedance is as follows. 13 K2 CO1

Line	Impedance (p.u)
1-2	0.06+j0.18
1-3	0.03+j0.09
2-3	0.08+j0.24

Neglect shunt capacitance of the line.

**OR**

- b) The single line diagram of a three phase power system is shown in Figure 1. Select a common base of 100MVA and 13.8KV on the generator side and construct the per unit impedance diagram. 13 K2 CO1

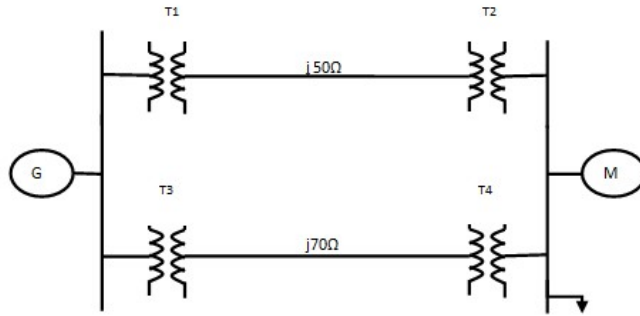


Figure 1

G: 90MVA, 13.8kV, X=18% ; T1:50MVA, 13.8/220kV, X=10%  
 T2:50MVA, 220/11kV, X=10% ; T3:50MVA, 13.8/132kV, X=10%  
 T4:50MVA, 132/11kV, X=10% ; M: 80MVA, 10.45kV, X=20%  
 Load: 57MVA, 0.8 p.f lagging at 10.45 kV

12. a) Discuss in detail about the algorithm for Gauss-Seidal load flow analysis and give the steps for its implementation when all the types of buses are present in the system. 13 K3 CO2

**OR**

- b) Explain in detail the algorithm for load flow solution by Newton-Raphson iterative method using Y bus and draw the flowchart for the same. 13 K3 CO2

13. a) A symmetrical fault occurs at bus 4 of the system through  $Z_f=j0.14 \text{ p.u}$  as shown in Figure 2. Compute the fault current, post fault voltages, and line flows. 13 K3 CO3

Generator  $G_1, G_2$  :100MVA, 20kV,  $X_1=15\%$ .  
 Transformer  $T_1, T_2$ :  $X_{leak}=9\%$ ,  
 Transmission line  $L_1, L_2$ :  $X_1=10\%$

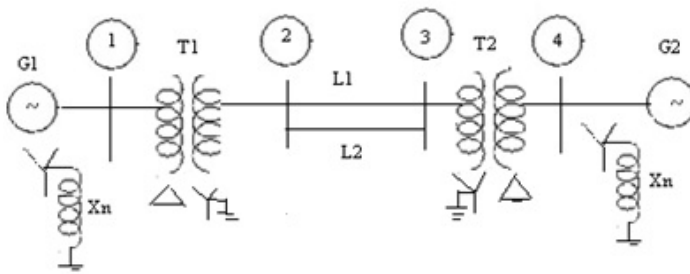


Figure 2

**OR**

- b) With the help of an algorithm explain how a symmetrical fault can be analyzed by using  $Z_{bus}$ . 13 K3 CO3

14. a) i) Derive the expression for fault current when a line to ground fault occurs on an unloaded generator. 10 K3 CO4  
 ii) Draw the connection of sequence networks for the same. 3 K3 CO4

OR

b) The sequence components of currents in a system are  $I_{a1}=8.334\angle 90^\circ$ ,  $I_{a2}=1.6668\angle 90^\circ$ ,  $I_{a0}=6.6672\angle 90^\circ$ . Find  $I_a, I_b, I_c$ . 13 K4 CO4

15. a) Derive the swing equation of a single machine connected to an infinite bus system. 13 K3 CO5

OR

b) Derive an expression for the critical clearing angle and clearing time to analyse the stability of a power system. 13 K3 CO5

**PART - C (1 × 15 = 15 Marks)**

16. a) Draw the reactance diagram for the given network in Figure 3 with a base of 50MVA and 13.8kV on generator  $G_1$  15 K3 CO1

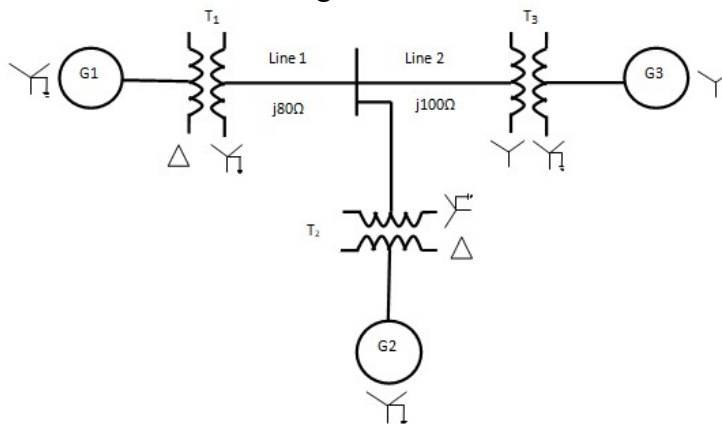


Figure 3

$G_1$ : 20MVA, 13.8kV,  $X''=20\%$ ;  $G_2$ : 30MVA, 18.0kV,  $X''=20\%$

$G_3$ : 30MVA, 20.0kV,  $X''=20\%$ ;

$T_1$ : 25MVA, 220/13.8 kV,  $X=10\%$

$T_2$ : 3Single phase unit each rated 10MVA, 127/18 kV,  $X=10\%$

$T_3$ : 35MVA, 220/22 kV,  $X=10\%$

OR

b) i) The moment of inertia of a 4 pole, 100 MVA, 11 kV, three phase, 0.8 power factor, 50 Hz turbo alternator is  $10000 \text{ kgm}^2$ . Calculate H, M. 8 K3 CO5

ii) A 50 Hz 8 pole generator rated at 80 MVA, 11kV has an inertia constant of 7 MJ/MVA. Find the moment of inertia M. 7 K3 CO5