

Reg. No.

Question Paper Code

12356

**B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023**

Fifth Semester

**Electrical and Electronics Engineering**  
**20EEPC501 - POWER SYSTEM ANALYSIS**  
 (Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

- |  | <i>Marks,</i><br><i>K-Level, CO</i> |
|--|-------------------------------------|
| 1. Show the importance of per unit computation.  | 2,K1,CO1                            |
| 2. A three phase transformer has a nameplate rating of 30MVA, 230Y/69Y kV with a leakage reactance of 10% and the transformer connection is Y-Y. Choosing a base of 30MVA and 230kV on high voltage side, calculate the reactance of the transformer in p.u. | 2,K3,CO1                            |
| 3. How the buses are classified and what are its types?  | 2,K2,CO2                            |
| 4. Why a slack bus is needed in load flow solution?  | 2,K2,CO2                            |
| 5. What do you understand by unsymmetrical faults in a power system?   | 2,K2,CO3                            |
| 6. Find the fault current if the prefault voltage at the fault point is 0.98 p.u.  | 2,K3,CO3                            |

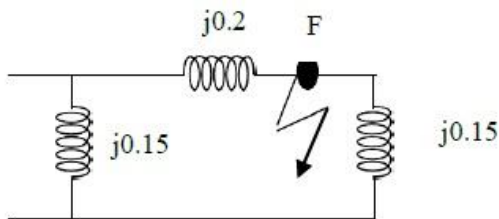


Figure 1

- |   |          |
|---|----------|
| 7. What are symmetrical components in a power system?   | 2,K2,CO4 |
| 8. Find the positive sequence current, if $I_a=18\angle 0^\circ\text{A}$ , $I_b=10\angle -30^\circ\text{A}$ , and $I_c=10\angle 30^\circ\text{A}$ . | 2,K3,CO4 |
| 9. Write the expression for maximum power transfer.   | 2,K2,CO5 |
| 10. What are the methods of improving transient stability?  | 2,K2,CO5 |

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) The single line diagram of a simple power system is shown in Fig. The rating of the generators and transformers are given below: 13,K2,CO1
- Generator 1: 25MVA, 6.6kV,  $X=0.2\text{p.u}$   
 Generator 2: 5MVA, 6.6kV,  $X=0.15\text{p.u}$   
 Generator 3: 30MVA, 13.2kV,  $X=0.15\text{p.u}$

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

**12356**

Transformer1: 30MVA, 6.9Δ/115Y kV, X=10%  
 Transformer2: 15MVA, 6.9Δ/115Y kV, X=10%  
 Transformer3: 3 single phase units each rated 10MVA, 6.9/69 kV, X=10%

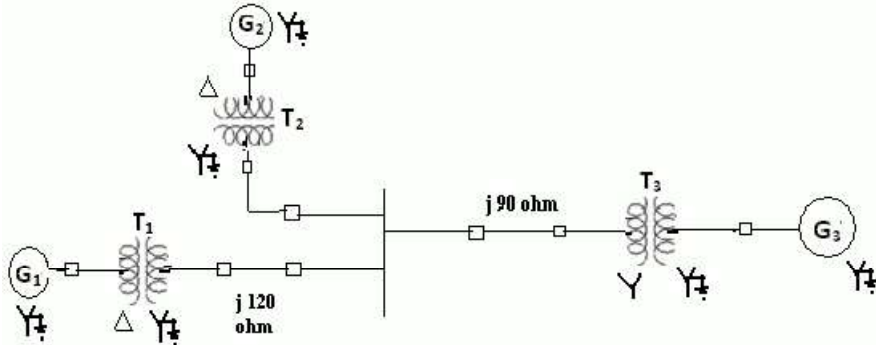


Figure 2

Construct the impedance diagram and mark all values in p.u choosing a base of 30MVA, 6.6kV in the generator 1 circuit.

OR

- b) Find the Y matrix of the sample power system as shown in fig. Data *13,K3,CO1* for this system is given in table.

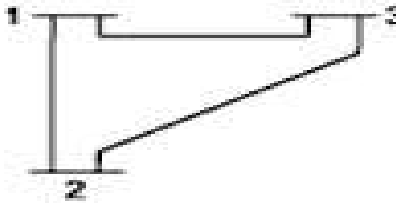


Figure 3

Bus code i-k	Impedance $Z_{ik}$	Line Charging Admittance $Y'$
1-2	$0.02+j0.06$	$j0.03$
1-3	$0.08+j0.24$	$j0.025$
2-3	$0.06+j0.18$	$j0.020$

12. a) With a neat flow chart explain the computational procedure for load flow solution using Gauss Seidal method when the system contains all types of buses. *13,K2,CO2*

OR

- b) Consider the power system with the following data: *13,K3,CO2*

$$Y_{\text{bus}} = \begin{pmatrix} -j12 & j8 & j4 \\ j8 & -j12 & j4 \\ j4 & j4 & -j8 \end{pmatrix}$$

Bus No.	Type	Generation		Load		Voltage	
		P	Q	P	Q	Magnitude	Angle
1	Slack	-	-	-	-	1.0	0
2	PV	5.0	-	0	-	1.05	-
3	PQ	0	0	3.0	0.5	-	-

Assume that the bus 2 can supply any amount of reactive power. With a flat voltage start, perform the first iteration of power flow analysis using NR method.

13. a) Explain how a symmetrical fault can be analyzed by using  $Z_{bus}$ . Also write the algorithm for the same. 13,K2,CO3

**OR**

- b) A 3 phase transmission line operating at 110kV and having impedance  $5+j20$  ohms is connected to the generating station through 15000 kVA step up transformer. Two alternators are connected to the bus bars. The ratings of the alternator are 10 MVA, 10%, 16 kV and 5 MVA, 7.5%, 16 kV. Calculate the short circuit MVA for a symmetrical fault at the load end of the transmission line. Take transformers reactance as 8%. 13,K3,CO3

14. a) Two synchronous machines are connected through three phase transformers to the transmission line as given in fig. The ratings and reactance of the machines and transformers are;

Machines 1 and 2: 100MVA, 20kV,  $X_d''=X_1=X_2=16\%$   $X_0=4\%$   
 $X_n=5\%$ :

Transformers T1 and T2:100 MVA; 20/345 kV;  $X=7\%$

Both the transformers are solidly grounded on two sides on a chosen base of 100MVA, 345kV in the transmission line circuit. The line reactances are  $X_1=X_2=8\%$  and  $X_0=40\%$ . The system is operating at nominal voltage without pre-fault currents when a bolted single to ground fault occurs on phase 'a' at bus 3. Determine the sub-transient current to ground at the fault.



Figure 4

**OR**

- b) Derive the expression for fault current in line to line fault on an unloaded generator and draw an equivalent network showing the interconnection of networks. 13,K2,CO4

15. a) Consider a single machine system shown in fig. Obtain the expression for critical clearing angle and critical clearing time when a three phase fault occurs at point F in the system. 13,K2,CO5

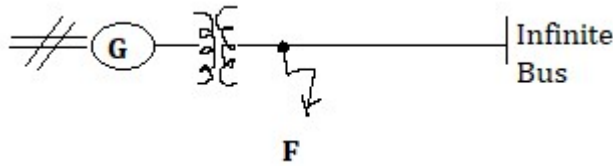


Figure 5

**OR**

- b) Derive the swing equation of a single machine connected to an infinite bus system. 13,K2,CO5

**PART - C (1 × 15 = 15 Marks)**

16. a) Two 11kV, 20 MVA, three phase star connected generators operate in parallel. The positive, negative and zero sequence reactance of each being respectively  $j0.18$ ,  $j0.15$ ,  $j0.10$  p.u. The star point of one of the generator is isolated and that of the other is earthed through a 2.0 ohm resistor. A single line to ground fault occurs at the terminals of one of the generators. Estimate (i) fault current (ii) current in grounded resistor and (iii) voltage across grounding resistor. 15,K3,CO4

**OR**

- b) Analyze the transient stability of the system for a sudden change in mechanical input. 15,K3,CO5