

Reg. No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12864
---------------------	-------

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024

Fifth Semester

Electrical and Electronics Engineering
20EEPC502 - POWER ELECTRONICS

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

	Marks	K- Level	CO
1. In TRIAC which of the modes the sensitivity of gate signal is high?	2	K2	CO1
2. Define latching current.	2	K1	CO1
3. Illustrate the function of freewheeling diodes in a controlled rectifier.	2	K2	CO2
4. Define overlap period or commutation period.	2	K2	CO2
5. Define by duty-cycle.	2	K1	CO3
6. Distinguish between PWM and FM control.	2	K2	CO3
7. Compare CSI and VSI.	2	K2	CO4
8. Define modulation index.	2	K1	CO4
9. What is a matrix converter?	2	K1	CO5
10. Compare integral cycle control and phase control in AC voltage controllers.	2	K2	CO5

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Explain the steady state and switching characteristics of MOSFET. 13 K2 CO1
- OR**
- b) Explain the structure and discuss the different modes of operation of TRIAC with the help of VI characteristics. 13 K2 CO1
12. a) Explain the operation of a single phase full converter with RLE load using relevant waveforms. Obtain the expressions for its average output voltage and RMS value of output voltage. 13 K2 CO2
- OR**
- b) Discuss the working of three phase six pulse converters with R load using relevant waveforms. Derive the average output voltage. 13 K2 CO2

13. a) Explain the working of boost converter with a neat sketch with waveform and derive the expression. 13 K2 CO3

OR

- b) Discuss the principle of operation of DC-DC class-E chopper with suitable waveforms. 13 K2 CO3

14. a) Describe the principle of operation of a 3 phase voltage source inverter with 180° conduction mode with necessary waveforms and circuits. Also obtain the expression for line to line voltage. 13 K2 CO4

OR

- b) Explain different types of PWM techniques to control the output voltage. 13 K2 CO4

15. a) Explain the operation of the step up and step down cyclo-converter with neat waveforms. 13 K2 CO5

OR

- b) A single phase voltage controller has input voltage of 230V 50Hz and a load of $R=15$ Ohm. For 6 cycles ON and 4 cycles OFF. Calculate (i) RMS output voltage (ii) Input power factor (iii) Average and RMS thyristor currents. 13 K2 CO5

PART - C (1× 15 = 15 Marks)

16. a) i) Explain the different method of voltage control adopted in inverter. 7 K2 CO4
ii) Explain the operation of multistage control of AC voltage controllers with a neat diagram. 8 K2 CO5

OR

- b) i) Explain the application of inverter in Induction heating. 8 K2 CO4
ii) Explain the operation of a 1-phase full wave AC voltage controller with R load using neat waveforms and derivation. 7 K2 CO5