

**B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2025**

Third Semester

**Electronics and Instrumentation Engineering**

**20EIPC303 - ANALOG ELECTRONIC CIRCUITS**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (MCQ) (10 × 1 = 10 Marks)**

Answer ALL Questions

	<i>Marks</i>	<i>K-Level</i>	<i>CO</i>
1. Diffusion capacitance in a diode is dominant under which condition? (a) Reverse bias      (b) Forward bias      (c) Zero bias      (d) Breakdown region	1	K1	CO1
2. In CE configuration, the input is applied between: (a) Base–Emitter      (b) Collector–Base      (c) Collector–Emitter      (d) None	1	K2	CO1
3. The drain current in a JFET depends primarily on: (a) Gate current      (b) Channel resistance      (c) VGS      (d) Temperature	1	K1	CO2
4. Class B amplifiers conduct for: (a) 90°      (b) 180°      (c) 270°      (d) 360°	1	K2	CO2
5. Which feedback reduces distortion? (a) Positive      (b) Negative      (c) Series only      (d) Shunt only	1	K1	CO3
6. Wien-bridge oscillator provides: (a) 0° shift      (b) 90° shift      (c) 180° shift      (d) 360° shift	1	K2	CO3
7. The input impedance of an ideal op-amp is: (a) Zero      (b) Finite      (c) Very high      (d) 1 Ω	1	K1	CO4
8. A comparator compares: (a) Two currents      (b) Two voltages      (c) Voltage & current      (d) None	1	K2	CO4
9. 555 Timer in astable mode generates: (a) Single pulse      (b) Square wave      (c) Ramp      (d) Sine wave	1	K1	CO5
10. LM317 is a: (a) Fixed regulator      (b) Switching regulator      (c) Variable regulator      (d) Zener regulator	1	K2	CO5

**PART - B (12 × 2 = 24 Marks)**

Answer ALL Questions

11. Draw the label the V–I characteristics of a PN junction diode.	2	K2	CO1
12. State any two advantages of voltage divider bias.	2	K1	CO1
13. Give the equation for drain current in a JFET.	2	K2	CO2
14. Write any two features of MOSFET.	2	K1	CO2
15. State Barkhausen criterion for oscillation.	2	K2	CO3
16. Mention two advantages of negative feedback.	2	K1	CO3
17. Write the ideal op-amp characteristics.	2	K1	CO4
18. Differentiate integrator from differentiator.	2	K2	CO4
19. Recall the applications of 555 timer.	2	K1	CO5
20. Mention two features of IC723 regulator.	2	K1	CO5
21. Define crossover distortion.	2	K1	CO3
22. Illustrate about slew rate.	2	K2	CO4

**PART - C (6 × 11 = 66 Marks)**

Answer ALL Questions

23. a) Explain Zener diode as voltage regulator with neat diagram. 11 K2 CO1  
**OR**  
b) Discuss BJT configurations with equations. 11 K2 CO1
24. a) Explain the working of a MOSFET amplifier with AC equivalent circuit. 11 K2 CO2  
**OR**  
b) Summarize class AB power amplifier with its crossover distortion. 11 K2 CO2
25. a) Outline RC phase shift oscillator with derivation for frequency of oscillation. 11 K2 CO3  
**OR**  
b) Rephrase the effect of negative feedback on gain, bandwidth and distortion w.r.t. any one LC phase shift oscillator. 11 K2 CO3
26. a) Interpret instrumentation amplifier with neat diagram. 11 K2 CO4  
**OR**  
b) Explain astable multivibrator using op-amp. 11 K2 CO4
27. a) Relate working of 555 timer in monostable mode. 11 K2 CO5  
**OR**  
b) Demonstrate the operation of LM317 adjustable voltage regulator. 11 K2 CO5
28. a) Extend the design of op-amp based peak detector. 11 K2 CO4  
**OR**  
b) With neat diagram explain sample and hold circuit. 11 K2 CO4