

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	13881
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2025**  
 Third Semester  
**Mechanical and Automation Engineering**  
**20EIPC304 - BASIC ELECTRONICS AND CONTROL SYSTEM**  
 Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (MCQ) (10 × 1 = 10 Marks)**

Answer ALL Questions

	<i>Marks</i>	<i>K- Level</i>	<i>CO</i>
1. Which of the following materials is most commonly used in semiconductor devices? (a) Copper (b) Silicon (c) Iron (d) Silver	1	K1	CO1
2. In an NPN transistor, current flows from: (a) Emitter to Collector (b) Collector to Emitter (c) Base to Collector (d) Collector to Base	1	K1	CO1
3. The output of an inverting amplifier is: (a) In phase with input (b) Out of phase by 90° (c) Out of phase by 180° (d) Random phase	1	K1	CO2
4. A Wien Bridge Oscillator is based on which type of feedback network? (a) RC bridge (b) LC tank circuit (c) Transformer coupling (d) Crystal	1	K1	CO2
5. The purpose of signal conditioning is to: (a) Generate signals (b) Modify signals for proper processing (c) Filter digital data (d) Convert DC to AC	1	K1	CO3
6. The sample and hold circuit is used to: (a) Smoothen DC voltage (b) Maintain a constant output voltage for a given time (c) Convert analog to digital (d) Amplify small signals	1	K1	CO3
7. A control system in which output has no effect on the control action is called a: (a) Closed-loop system (b) Open-loop system (c) Feedback system (d) Regenerative system	1	K1	CO4
8. In a mechanical translational system, the analogy of electrical current is: (a) Force (b) Velocity (c) Displacement (d) Spring	1	K1	CO4
9. The time response of a control system consists of: (a) Only transient response (b) Only steady-state response (c) Transient and steady-state responses (d) Frequency response only	1	K1	CO5
10. The damping ratio of a second-order system determines: (a) Final value (b) Type of transient response (c) Static error (d) Bandwidth	1	K1	CO5

**PART - B (12 × 2 = 24 Marks)**

Answer ALL Questions


11. Define intrinsic and extrinsic semiconductors.	2	K1	CO1
12. What are the advantages of MOSFET over JFET?	2	K1	CO1
13. Write the voltage gain expression for an inverting amplifier.	2	K1	CO2
14. State Barkhausen criterion for sustained oscillations.	2	K1	CO2
15. Illustrate the meaning of impedance matching.	2	K2	CO3
16. State any two applications of ADC.	2	K1	CO3
17. What are the basic elements of a control system?	2	K1	CO4
18. Define signal flow graph.	2	K1	CO4

- |   |   |    |     |
|---|---|----|-----|
| 19. Define Peak time.   | 2 | K1 | CO5 |
| 20. What are the factors to determine the steady state error? | 2 | K1 | CO5 |
| 21. Draw the energy band structure of P- type semiconductor.  | 2 | K1 | CO1 |
| 22. Define signal level and bias changes.                     | 2 | K1 | CO3 |

**PART - C (6 × 11 = 66 Marks)**


Answer ALL Questions

- |           |  |    |    |     |
|-----------|--|----|----|-----|
| 23. a)    | With a neat diagram explain the working of a PN junction diode in forward bias and reverse bias and show the effect of temperature on its V-I characteristics.   | 11 | K2 | CO1 |
| <b>OR</b> |  |    |    |     |
| b) (i)    | Demonstrate the V-I characteristics of Zener diode.  | 5  | K2 | CO1 |
| (ii)      | Explain with neat sketch of working and construction of PNP transistor.  | 6  | K2 | CO1 |
| 24. a)    | Outline the need for an instrumentation amplifier? Give a detailed analysis for the same. Explain about any one industrial application of instrumentation amplifier.   | 11 | K2 | CO2 |
| <b>OR</b> |  |    |    |     |
| b)        | With a neat circuit diagram, describe the working of a Wien bridge oscillator. Derive an expression for the resonant frequency and condition for maximum oscillation. Give its advantages and disadvantages. | 11 | K2 | CO2 |
| 25. a)    | Apply the concept of successive approximation ADC to a digital voltmeter design. Explain its working, advantages, disadvantages.   | 11 | K3 | CO3 |
| <b>OR</b> |  |    |    |     |
| b)        | Apply the concept of R/2R ladder DAC to design a digital-to-analog converter for audio signal generation. Explain its working, merits, demerits, and practical usage.  | 11 | K3 | CO3 |
| 26. a)    | Write the differential equations of the mechanical system shown in fig .and draw the force-voltage and force -current analogous circuit and verify by writing Mesh and Nodal equations.                      | 11 | K3 | CO4 |

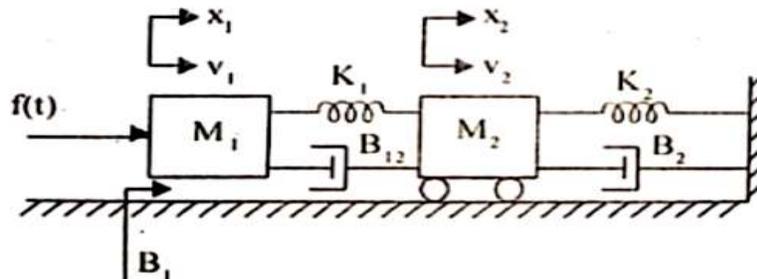

**OR**

- |    |  |    |    |     |
|----|--|----|----|-----|
| b) | Calculate the overall gain $C(s)/R(s)$ for the signal flow graph shown in fig. | 11 | K3 | CO4 |
|----|--|----|----|-----|

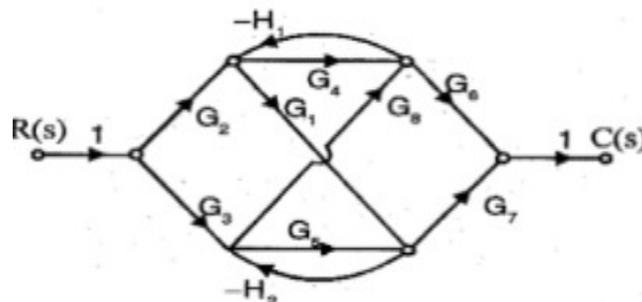


27. a) Derive the expression and draw the response of second order system for under damped case with unit step input. 11 K3 CO5

**OR**

- b) Derive the expressions for Time domain specifications with unit step input. 11 K3 CO5

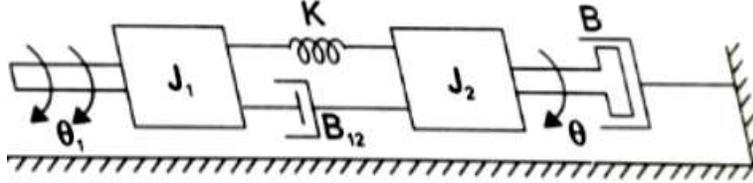28. a) Find the Transfer Function of the given Mechanical System. 11 K3 CO4



**OR**

- b) Consider the unity feedback system with a closed loop transfer function  $C(s)/R(s) = Ks + b/s^2 + as + b$ . Determine open loop transfer function  $G(s)$ . Show that steady state error with unit ramp input is given by  $(a-k)/b$ . 11 K3 CO4