

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12340
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023**  
Third Semester  
**Mechanical and Automation Engineering**  
**20EIPC304 - BASIC ELECTRONICS AND CONTROL SYSTEM**  
(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

- |   | <i>Marks,<br/>K-Level, CO</i> |
|---|-------------------------------|
| 1. Differentiate between intrinsic and extrinsic semiconductor.     | 2,K2,CO1                      |
| 2. Give the two important characteristics of JFET.                  | 2,K2,CO1                      |
| 3. Mention the characteristics of an ideal op-amp.                  | 2,K1,CO2                      |
| 4. Define CMRR of an op-amp.  | 2,K1,CO2                      |
| 5. Draw a sample and hold circuit.                                  | 2,K2,CO3                      |
| 6. List out the direct type ADCs.                                   | 2,K1,CO3                      |
| 7. Distinguish between open loop and closed loop system.            | 2,K2,CO4                      |
| 8. Define transfer function.  | 2,K1,CO4                      |
| 9. What is weighing function?                                       | 2,K1,CO5                      |
| 10. How the system is classified depending on the value of damping? | 2,K2,CO5                      |

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

- |   |           |
|---|-----------|
| 11. a) With a neat diagram explain the working of a PN junction diode in forward bias and reverse bias and show the effect of temperature on its V-I characteristics. | 13,K2,CO1 |
| <b>OR</b>   |           |
| b) Explain the working of the Common Emitter transistor and obtain the characteristics.   | 13,K2,CO1 |
| 12. a) (i) Explain Inverting amplifier with neat sketch.  | 5,K2,CO2  |
| (ii) Explain Non-inverting amplifier with neat sketch.  | 5,K2,CO2  |
| (iii) Mention the applications of Operational amplifier.  | 3,K1,CO2  |
| <b>OR</b>   |           |
| b) Explain Differentiator with neat sketch.   | 13,K2,CO2 |
| 13. a) (i) Explain Sample and hold circuit with neat sketch.  | 7,K2,CO3  |
| (ii) Explain Peak detector with neat sketch.  | 6,K2,CO3  |


*K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create*

**12340**

OR


- b) Explain in details about successive approximation and dual slope type ADC with neat diagram. 13,K2,CO3

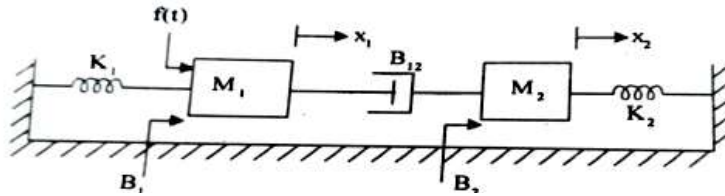14. a) Compute the differential equations governing the mechanical system shown in fig. and determine the transfer function. 13,K3,CO4



OR

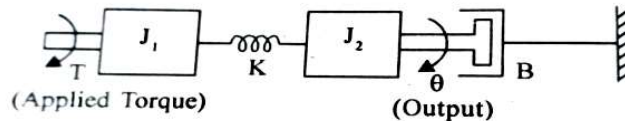- b) Compute the differential equations governing the mechanical rotational system shown in fig. and determine the transfer function. Draw the torque-voltage and torque-current electrical analogous circuits 13,K3,CO4




15. a) Derive the response of undamped second order system for unit step input. 13,K2,CO5

OR

- b) Derive the response of first order system for unit step input. 13,K2,CO5

**PART - C (1 × 15 = 15 Marks)**

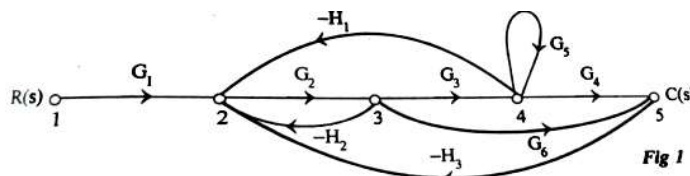16. a) Calculate the overall gain  $C(s)/R(s)$  for the signal flow graph shown in fig. 15,K3,CO4



OR

- b) The response of a servomechanism is  $c(t) = 1 + 0.2e^{-60t} - 1.2e^{-10t}$  when subject to a unit step input. Obtain an expression for closed loop transfer function. Determine the undamped natural frequency and damping ratio. 15,K2,CO5