

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12747
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024**

Sixth Semester

**Electronics and Instrumentation Engineering**

**20EIPC603 - POWER ELECTRONICS, DRIVES AND CONTROL**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

	<i>Marks</i>	<i>K- Level</i>	<i>CO</i>
1. Indicate the basic operating principle of Bipolar Junction Transistor (BJT) in saturation mode.	2	K2	CO1
2. State the function of gate turn-off thyristor (GTO).	2	K1	CO1
3. Identify the factors affecting the performance of AC voltage controllers.	2	K2	CO2
4. Name different types of single-phase rectifiers.	2	K1	CO2
5. Define the term duty cycle and its importance in chopper operation.	2	K1	CO3
6. Why forced commutation is used in DC chopper?	2	K2	CO3
7. Define the term "inverter" and its function in power electronics.	2	K1	CO4
8. Indicate the advantages of Pulse width modulation (PWM) technique used in an inverter	2	K2	CO4
9. Name the principles behind voltage/frequency (V/F) control of drives.	2	K1	CO5
10. List the methods used for electrical braking in DC and AC machines.	2	K1	CO5

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) i) Compare the operating principles of IGBT with power MOSFET.	7	K2	CO1
ii) Evaluate the advantages and disadvantages of using TRIAC over SCR in AC power control applications.	6	K2	CO1
<b>OR</b>			
b) i) Sketch the typical V-I characteristics of power diode and label the important regions in detail.	7	K2	CO1
ii) Describe the differences between series and parallel operation of power devices.	6	K2	CO1
12. a) i) Explain how to calculate the average output voltage of a single-phase half-wave rectifier with necessary diagrams.	7	K2	CO2
ii) In a three-phase fully controlled rectifier, explain how the firing angle can be adjusted to control the output DC voltage.	6	K2	CO2

*K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create*

**12747**

**OR**

- b) Explain the operation of a single-phase full converter with RLE load using relevant waveforms. Obtain the expression for its average output voltage and RMS value of output voltage 13 K2 CO2

13. a) Describe the operation of buck-boost regulators with necessary diagram and waveforms. 13 K2 CO3

**OR**

- b) Write about different classes of choppers in terms of characteristics, efficiency and performance. 13 K2 CO3

14. a) i) Explain the working principle of a single-phase full-bridge inverter circuit with a DC source. 10 K2 CO4

- ii) Interpret the concept of current source inverters. 3 K2 CO4

**OR**

- b) Describe the functioning of resonant inverters including series ZVS, and ZCS types. 13 K2 CO4

15. a) Elucidate the operation of rectifier and chopper control techniques in DC drives. 13 K2 CO5

**OR**

- b) Design and explain the block diagram representation of a closed-loop control scheme for an AC drive. 13 K2 CO5

**PART - C (1× 15 = 15 Marks)**

16. a) Draw and explain the schematic block diagram of SMPS and mention its advantages over linear power supply. 15 K5 CO3

**OR**

- b) Evaluate the performance of various PWM techniques in terms of harmonic distortion and efficiency with suitable case study. 15 K5 CO4