

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12545
---------------------	-------

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023
 First Semester
Computer Science and Business Systems
20ESEE105 - PRINCIPLES OF ELECTRICAL ENGINEERING
 (Regulations 2020)

Duration: 3 Hours


Max. Marks: 100

PART - A (10 × 2 = 20 Marks)
 Answer ALL Questions

- | | <i>Marks,</i> |
|--|--------------------|
| | <i>K-Level, CO</i> |
| 1. A 10 watt resistor has a value of 120 ohms. What is the rated current through the resistor? | 2,K2,CO1 |
| 2. Compare Series and Parallel resistive Circuit. | 2,K2,CO1 |
| 3. Write the steps to convert star to delta network. | 2,K1,CO2 |
| 4. What are the advantages of Thevenin's theorem? | 2,K1,CO2 |
| 5. Define form factor and peak factor in AC circuit Analysis. | 2,K1,CO3 |
| 6. Illustrate the significance power factor. | 2,K1,CO3 |
| 7. A parallel plate capacitor has plates 1mm apart and a dielectric with relative permittivity of 3.39. Find electric intensity and voltage between the plates if the charge density is $3 \times 10^{-4} \text{ C/m}^2$. | 2,K2,CO4 |
| 8. What is the principle of operation of a single phase transformer? | 2,K1,CO4 |
| 9. What is meant by indicating type instrument and give example? | 2,K1,CO5 |
| 10. List the various properties of good transducers. | 2,K1,CO5 |

PART - B (5 × 13 = 65 Marks)
 Answer ALL Questions

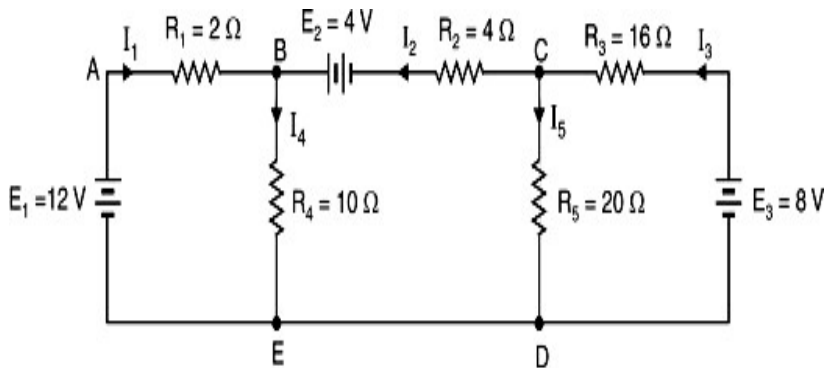
11. a) Find the currents using nodal analysis. 13,K2,CO1



OR


b) Find the branch current in the network by using Mesh analysis.

13,K2,CO1

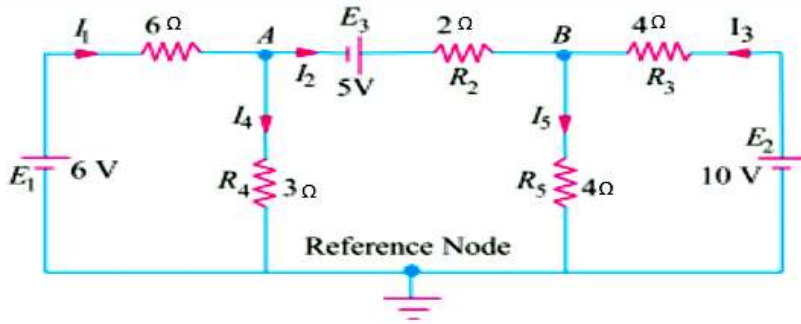

12. a) Find the Norton's equivalent circuit and solve for load voltage and load current.


13,K2,CO2

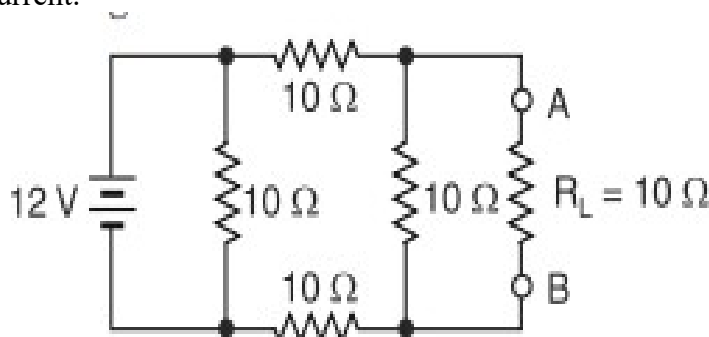

OR

b) Find the resistances between A and B, B and C & C and A by using delta / star transformation.

13,K2,CO2

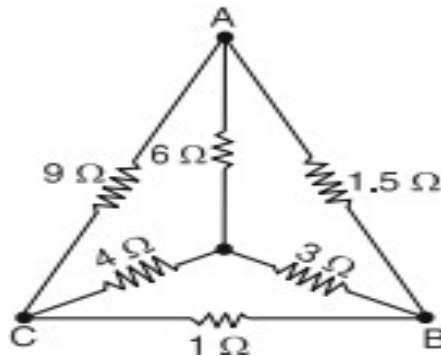

13. a) Explain the operation of RLC series AC circuit with relevant phasor diagram and derive the formulas for phase angle, Impedance, Admittance and power. And also draw the power curve of the RLC Series AC circuit.

13,K2,CO3

OR

b) A 230 V, 50 Hz ac supply is applied to a coil of 0.06 H inductance and 2.5ohm resistance connected in series with a 6.8 μF capacitor. Infer (i) impedance (ii) current (iii) phase angle between current and voltage (iv) power factor and (v) power consumed.

13,K2,CO3

14. a) Show the similarities and dissimilarities between magnetic and electric circuits. *13,K2,CO4*

OR

- b) Derive the expression for discharging of capacitor with relevant diagrams. *13,K2,CO4*

15. a) Explain the construction and working of PMMC. *13,K2,CO5*

OR

- b) Explain the necessity of earthing and its two types. *13,K2,CO5*

PART - C (1 × 15 = 15 Marks)

16. a) (i) Explain the core and shell type transformer. *8,K2,CO4*

- (ii) Construct the different types of measuring instruments available and the torque development in them. *7,K2,CO5*

OR

- b) (i) Derive an expression for capacitor with composite medium. *8,K2,CO4*

- (ii) Explain the working and measurement of single phase wattmeter. *7,K2,CO5*