

[illegible]

Question Paper Code	13310
----------------------------	--------------

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2024

First Semester

Computer Science and Business Systems

20ESEE105 - PRINCIPLES OF ELECTRICAL ENGINEERING

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (MCQ) (20 × 1 = 20 Marks)

Answer ALL Questions

PART - A (MCQ) (20 × 1 = 20 Marks)				Marks	K – Level	CO
Answer ALL Questions						
1.	What is the unit of electric current? (a) Ohm (b) Volt (c) Ampere (d) Watt			1	K1	CO1
2.	Which law is used in nodal analysis of circuits? (a) Ohm's Law (b) Kirchhoff's Current Law (KCL) (c) Faraday's Law (d) Coulomb's Law			1	K1	CO1
3.	What is a practical voltage source characterized by? (a) Ideal voltage with no resistance (b) Constant current supply (c) Internal resistance (d) Dependence on power			1	K1	CO1
4.	What is the maximum power transfer theorem used to determine? (a) Voltage in a circuit (b) The load resistance for maximum power transfer (c) Current in a short circuit (d) Power factor improvement			1	K1	CO1
5.	Which transformation converts a delta circuit to a star circuit? (a) Norton Transformation (b) Star-Delta Transformation (c) Thevenin's Transformation (d) Superposition Theorem			1	K1	CO2
6.	Norton's theorem is associated with converting a complex network into what? (a) A single voltage source and series resistance (b) A single current source and parallel resistance (c) A combination of series and parallel components (d) None of the above			1	K1	CO2
7.	In an AC circuit, what is the ratio of peak to RMS voltage called? (a) Peak factor (b) Form factor (c) Power factor (d) Impedance			1	K1	CO2
8.	Which component is used to oppose changes in current in AC circuits? (a) Resistor (b) Capacitor (c) Inductor (d) Transformer			1	K1	CO2
9.	In three-phase systems, the type of connection used for a balanced load is: (a) Delta-Delta (b) Star-Star (c) Both Delta-Delta and Star-Star (d) Star-Delta only			1	K1	CO3
10.	What does the electrostatic field strength depend on? (a) Distance and mass (b) Charge and distance (c) Voltage and resistance (d) Current and time			1	K1	CO3
11.	The primary unit of capacitance is: (a) Farad (b) Coulomb (c) Volt (d) Ohm			1	K1	CO3
12.	Faraday's Law is related to which phenomenon? (a) Electrostatic force (b) Electromagnetic induction (c) Power dissipation (d) Capacitance			1	K1	CO3
13.	Which of the following is a piezoelectric sensor primarily used to measure? (a) Temperature (b) Pressure (c) Humidity (d) Voltage			1	K1	CO4
14.	A thermocouple generates voltage in response to changes in: (a) Light (b) Sound (c) Temperature (d) Humidity			1	K1	CO4
15.	Earthing is essential in electrical systems primarily for: (a) Enhancing efficiency (b) Safety and protection (c) Voltage regulation (d) Load balancing			1	K1	CO4

- | | |
|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------|
| 16. The unit of electric power in single-phase systems is: | 1 K1 CO4 |
| (a) Volt (b) Watt (c) Ohm (d) Coulomb | |
| 17. The principle of operation of a transformer is based on which law? | 1 K1 CO5 |
| (a) Ohm's Law (b) Faraday's Law of Electromagnetic Induction
(c) Coulomb's Law (d) Kirchhoff's Voltage Law | |
| 18. Mutual inductance is the property of two coils to: | 1 K1 CO5 |
| (a) Resist current flow
(b) Produce magnetic flux
(c) Induce voltage due to a change in current in another coil
(d) Store electrical energy | |
| 19. Ampere's Law is primarily used to calculate: | 1 K1 CO5 |
| (a) Magnetic field due to a current-carrying conductor (b) Electric field due to a charge
(c) Capacitance of a capacitor (d) Voltage drop across a resistor | |
| 20. The unit of magnetic flux is: | 1 K1 CO5 |
| (a) Tesla (b) Weber (c) Henry (d) Farad | |

PART - B (10 × 2 = 20 Marks)


Answer ALL Questions

- | | |
|-------------------------------------------------------------------------------------------|----------------|
| 21. Compare active and passive elements. | 2 K2 CO1 |
| 22. Define terms Node & branch. | 2 K1 CO1 |
| 23. List the steps to solve the Thevenin's Theorem. | 2 K1 CO2 |
| 24. Define maximum power transfer theorem. | 2 K1 CO2 |
| 25. Name the concept of impedance. | 2 K1 CO3 |
| 26. Define the active and reactive powers. | 2 K1 CO3 |
| 27. Recall on capacitor composite. | 2 K1 CO4 |
| 28. Define Ampere's Law. | 2 K1 CO4 |
| 29. Compare between sensors and transducers. | 2 K2 CO5 |
| 30. Explain the concept of mutual inductance and its significance in electrical circuits. | 2 K2 CO5 |

PART - C (6 × 10 = 60 Marks)


Answer ALL Questions

- | | |
|------------------------------------------------------------------------------------|-----------------|
| 31. a) Infer the current supplied by the batteries in the circuit shown in Figure. | 10 K2 CO1 |
|------------------------------------------------------------------------------------|-----------------|

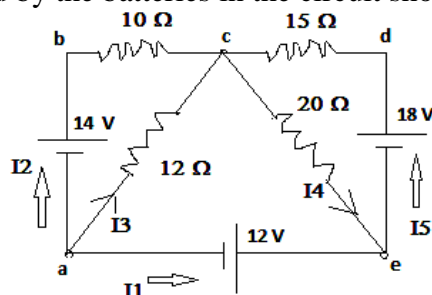

OR

- | | |
|--------------------------------------------------------|-----------------|
| b) Infer the mesh currents in the circuit shown below. | 10 K2 CO1 |
|--------------------------------------------------------|-----------------|

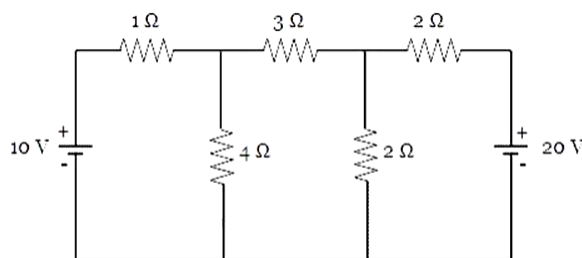


- | | |
|----------------------------------------------------------------------------------------------------------------------|-----------------|
| 32. a) Develop the step by step procedure to the Norton's Theorem Formula. Also State the merits and demerits of it. | 10 K3 CO2 |
|----------------------------------------------------------------------------------------------------------------------|-----------------|

OR


b) Identify the current flowing through $20\ \Omega$ using the superposition theorem.

10 K3 CO2

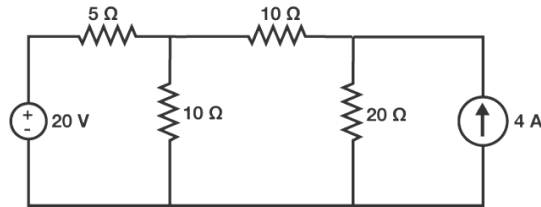

33. a) Two parallel circuits comprising of (i) a coil of resistance of $20\ \Omega$ and inductance of $0.07\ \text{H}$ and (ii) a resistance of $50\ \Omega$ in series with a condenser of capacitance $60\ \mu\text{F}$ are connected across $230\ \text{V}$, $50\ \text{Hz}$. Solve for the main current and power factor of the arrangement.

10 K3 CO3

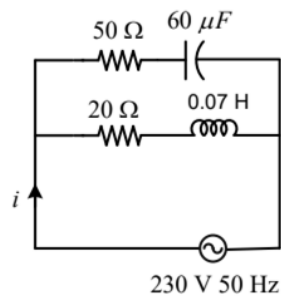

OR

- b) Three identical coils having resistance of $10\ \Omega$ and an inductance of $0.05\ \text{H}$ each are connected in star across a $3\ \phi$, $400\ \text{V}$ $50\ \text{Hz}$ balanced supply. Identify the line current and the power consumed. What will be the reading of two wattmeters connected to measure the total power?

10 K3 CO3

34. a) Outline an expression for energy of a charged capacitor. Show that the dielectric in between the plates of a parallel plate capacitor experiences a force and derive an equation for it.

10 K2 CO4

OR

- b) Show the role of dielectric materials in capacitors and how they impact the overall capacitance. Provide examples of applications where dielectric properties are critical.

10 K2 CO4

35. a) Outline the various types of drawing used for electrical wiring. Explain in detail.

10 K2 CO5

OR

- b) Explain the Construction and working principle of piezoelectric transducers and thermocouples.

10 K2 CO5

36. a) i) Compare between self-inductance and mutual inductance in an electromagnetic circuit.

5 K2 CO4

- ii) Explain the Working of PMMC.

5 K2 CO5

OR

- b) i) Explain the principles behind the operation of a single-phase transformer.

5 K2 CO4

- ii) Explain Earthing and its types.

5 K2 CO5