

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12653
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024**

Second Semester

**Mechanical Engineering**

(Common to Mechanical and Automation Engineering )

**20ESEE201 - ELECTRICAL TECHNOLOGY WITH LABORATORY**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**


Answer ALL Questions

- |   | Marks | K-<br>Level | CO  |
|---|-------|-------------|-----|
| 1. Define the term node and junction.   | 2     | K1          | CO1 |
| 2. Define active and passive elements.  | 2     | K1          | CO1 |
| 3. A 100 V lamp has a hot resistance of 250 Ω. Find the current taken by the lamp and its power rating in watts. Calculate also the energy it will consume in 24 hours. | 2     | K2          | CO2 |
| 4. List some applications of maximum power transfer theorem.  | 2     | K1          | CO2 |
| 5. What is back EMF or counter EMF?   | 2     | K1          | CO3 |
| 6. What is self and separately excited DC generator?  | 2     | K1          | CO3 |
| 7. List the applications of 3-phase induction motor.  | 2     | K1          | CO4 |
| 8. What are the advantages of salient pole type construction used for synchronous machines?   | 2     | K1          | CO4 |
| 9. What is the necessity of a starter?  | 2     | K1          | CO5 |
| 10. List the different types of braking.  | 2     | K1          | CO5 |

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

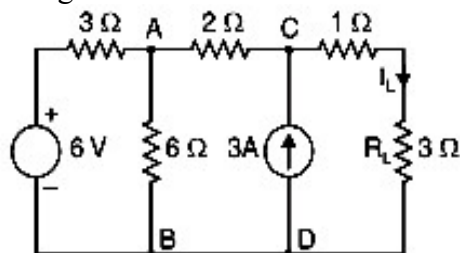11. a) Make use of source conversion technique, find the load current  $I_L$  in the circuit shown in Fig. 13 K3 CO1




**OR**


- b) Identify to determine the current flow through the individual loops using Mesh Analysis. 13 K3 CO1

*K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create*

**12653**

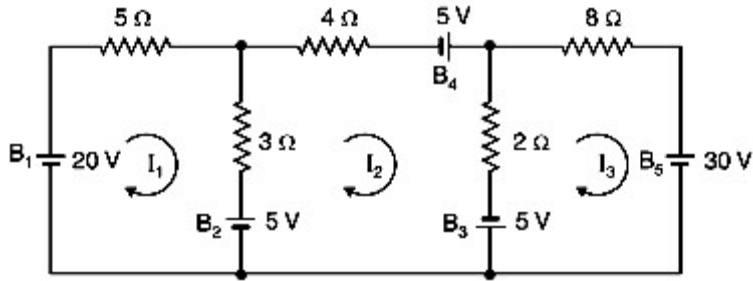


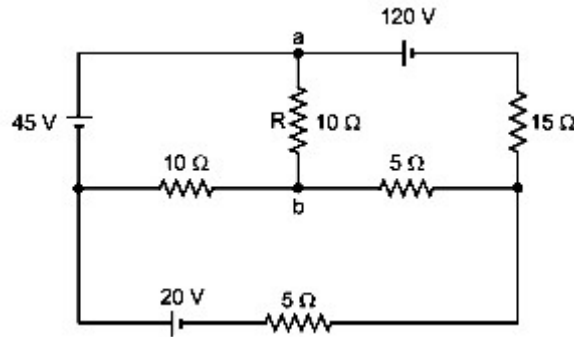12. a) Identify to find the current through the resistance R connected between **a** and **b** using Thevenin's theorem. 13 K3 CO2



**OR**

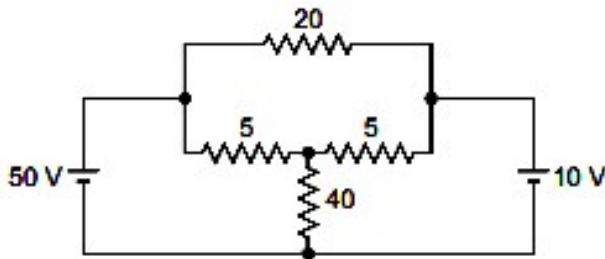- b) Apply the superposition theorem to find the current in the 40 ohm resistor. All resistances are in ohms. 13 K3 CO2



13. a) Explain the construction and working of a single-phase transformer. 13 K2 CO3

**OR**

- b) i) Develop the torque equation of DC machine which is used in steel mills. 7 K3 CO3  
 ii) Classify the different types of DC generator in details. 6 K2 CO3

14. a) Explain the construction and principle of operation of synchronous machine with a neat sketch. 13 K2 CO4

**OR**

- b) Develop the expression for torque, slip and draw speed torque characteristics in Induction Motor. 13 K3 CO4

15. a) A 10 pole DC shunt generator with 800 wave connected conductors and running at 600 rpm supplies a load of  $15\ \Omega$  resistance at a terminal voltage of 240V. The armature resistance is  $0.28\ \Omega$  and field resistance is  $240\ \Omega$ . Determine the armature current, the induced emf and flux per pole. 13 K3 CO5

**OR**

- b) Illustrate about different types of electric drives and its applications to industry. 13 K2 CO5

**PART - C (1 × 15 = 15 Marks)**

16. a) i) Explain the three-point starter for DC motor. 8 K2 CO6  
ii) Classify the various starting methods of induction motors. 7 K2 CO6

**OR**

- b) Infer how an induction motor is brought to stop by (i) Plugging and (ii) dynamic braking 15 K2 CO6