

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023

Second Semester

Civil Engineering

20ESEE202 - BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)


Answer ALL Questions

- | | <i>Marks,</i>
<i>K-Level, CO</i> |
|---|-------------------------------------|
| 1. Define Ohm's Law. | 2,K1,CO1 |
| 2. Compare series and parallel circuit. | 2,K2,CO1 |
| 3. Define power factor. | 2,K1,CO2 |
| 4. Interpret any four advantages of three phase system. | 2,K2,CO2 |
| 5. What is back e.m.f. of DC motor? | 2,K1,CO3 |
| 6. Why transformers are rated in KVA instead of KW? | 2,K1,CO3 |
| 7. Mention the applications of Zener Diode. | 2,K1,CO4 |
| 8. Draw the Drain Characteristics of JFET. | 2,K1,CO4 |
| 9. What is LVDT? | 2,K1,CO5 |
| 10. Differentiate sensors and transducers. | 2,K1,CO6 |

PART - B (5 × 13 = 65 Marks)


Answer ALL Questions

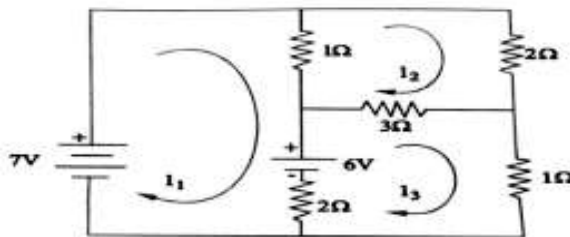11. a) Use mesh analysis to determine the three mesh currents in the circuit. 13,K2,CO1



OR

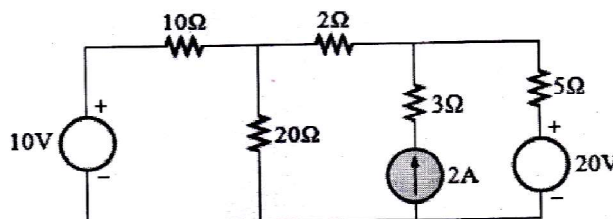- b) Find the voltage across 2Ω resistor by using superposition theorem. 13,K2,CO1



12. a) Illustrate the wiring materials and its accessories used for House wiring. *13,K3,CO2*

OR

- b) Explain in detail about three phase balanced circuits. *13,K2,CO2*

13. a) Explain the principle of operation of DC motor and derive its torque equation. *13,K2,CO3*

OR

- b) Explain the principle working of Single phase Induction motor. *13,K2,CO3*

14. a) Illustrate the construction and working of Bipolar Junction Transistor (BJT). Also draw the input and output characteristics of the common emitter configuration. *13,K2,CO4*

OR

- b) Explain the working of an Op-amp as an inverting and non-inverting amplifier. *13,K2,CO4*

15. a) Elaborate with a neat sketch, the construction and working principle of piezoelectric transducer and list its advantages and disadvantages. *13,K2,CO6*

OR

- b) Explain three phase power measurement using two wattmeter methods with necessary circuit diagram, phasor diagrams and expressions. *13,K2,CO5*

PART - C (1 × 15 = 15 Marks)

16. a) Explain the working principle and construction of single phase transformer and derive its emf equation. *15,K5,CO3*

OR

- b) With a neat sketch explain about the working of Permanent Magnet Moving Coil (PMMC) and derive its torque equation. *15,K5,CO6*