

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12649
---------------------	-------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024**

Second Semester

**Civil Engineering**

**20ESEE202 - BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**


Answer ALL Questions

- |   | Marks | K-Level | CO  |
|---|-------|---------|-----|
| 1. Define Kirchhoff's Current Law and Voltage Law.                | 2     | K1      | CO1 |
| 2. State Thevenins theorem.                                       | 2     | K1      | CO1 |
| 3. Recall about the industrial wiring.                            | 2     | K1      | CO2 |
| 4. Define apparent power.   | 2     | K1      | CO2 |
| 5. Mention the function of carbon brush in DC machine.            | 2     | K1      | CO3 |
| 6. What are the various losses in DC Machines?                    | 2     | K1      | CO3 |
| 7. Define Fermi level.  | 2     | K1      | CO4 |
| 8. List the types of ADC.   | 2     | K1      | CO4 |
| 9. Classify-transducer.   | 2     | K2      | CO5 |
| 10. What are the suitable materials for piezoelectric transducer? | 2     | K1      | CO5 |

**PART - B (5 × 13 = 65 Marks)**


Answer ALL Questions

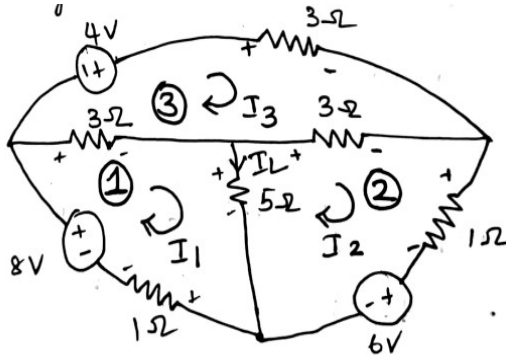11. a) Solve the given circuit and find the values of I and R. 13 K3 CO1



**OR**

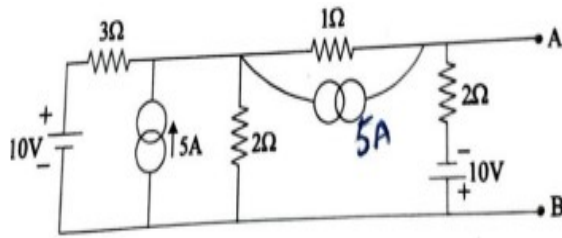- b) Make use of Thevenin's equivalent for the network between A and B and compute the values. 13 K3 CO1



12. a) A coil of resistance  $10\Omega$  and an inductance of  $0.1\text{H}$  is connected in series with a capacitance of  $150\mu\text{F}$  across a  $200\text{V}, 50\text{ Hz}$  supply calculate  
 a) the inductive reactance b) the capacitive reactance c) the net reactance  
 d) the current e) the power factor of the circuit f) also find voltage across R, L and C. 13 K2 CO2

**OR**

- b) Illustrate the wiring materials and its accessories used for House wiring. 13 K2 CO2
13. a) Explain the working principle and construction of single phase transformer and derive its emf equation. 13 K2 CO3

**OR**

- b) i) Derive the emf equation of the DC generator. 7 K2 CO3  
 ii) Explain about DC separately excited DC generator. 6 K2 CO3
14. a) Explain the input and output characteristics of a CE transistor configuration. 13 K2 CO4

**OR**

- b) Enumerate about Inverting and Non Inverting operational amplifier with neat diagram. 13 K2 CO4
15. a) Illustrate with neat diagram about Linear Variable Differential Transformer and discuss its waveform. 13 K2 CO5

**OR**

- b) Describe the working principle and construction of Capacitive and Piezo electric Transducer. 13 K2 CO5

**PART - C ( $1 \times 15 = 15$  Marks)**

16. a) Explain the working principle and construction of MI-Attraction and Repulsion type Instrument. 15 K2 CO6

**OR**

- b) With a neat sketch explain about the working of Permanent Magnet Moving Coil (PMMC) and derive its torque equation. 15 K2 CO6