

Reg. No.

Question Paper Code

12531

**B.E. / B.Tech. / M.Tech. - DEGREE EXAMINATIONS, NOV/DEC 2023**

Second Semester

**Information Technology**

(Common to Computer Science and Engineering, Computer Science and Engineering (IoT), Computer Science and Engineering (Cyber Security) &amp; M.Tech. - Computer Science and Engineering)

**20ESIT203 - DIGITAL PRINCIPLES AND SYSTEM DESIGN**

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

- |   | <i>Marks,</i><br><i>K-Level, CO</i> |
|---|-------------------------------------|
| 1. Prove the following using Demorgan's theorem<br>[[X+Y]'+(X+Y)']'=X+Y | 2,K1,CO1                            |
| 2. Represent XOR gate using only 4-NAND gates.                          | 2,K2,CO1                            |
| 3. Define self-complementing code.                                      | 2,K1,CO2                            |
| 4. Trace the truth table for BCD to Excess-3 code converter.            | 2,K2,CO2                            |
| 5. Differentiate Mealy and Moor machines.                               | 2,K2,CO3                            |
| 6. Give the characteristics table and equation of JK flipflop.          | 2,K2,CO3                            |
| 7. Define cycles and races.   | 2,K1,CO4                            |
| 8. Define Essential Hazard.   | 2,K1,CO4                            |
| 9. Describe about Shared Row method.                                    | 2,K2,CO5                            |
| 10. List any two drawbacks of asynchronous circuits.                    | 2,K2,CO5                            |

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

- |  |           |
|--|-----------|
| 11. a) (i) Represent the Boolean function in SOP and POS Form. $F(A,B,C,D)=\sum m(0,1,2,5,8,9,10)$                   | 7,K2,CO1  |
| (ii) Plot the following Boolean function in k-map and simplify it.<br>$F(W,X,Y,Z)=\sum m(0,1,2,4,5,6,8,9,12,13,14).$ | 6,K2,CO1  |
| <b>OR</b>  |           |
| b) Indicate the Minimized expression using K-map method<br>$F=\sum m(0,1,9,15,24,29,30) +\sum d(8,11,31).$           | 13,K2,CO1 |
| 12. a) Develop a code converter that converts a 8421 to BCD code.  | 13,K3,CO2 |
| <b>OR</b>  |           |
| b) Develop a logic circuit that accepts a 4bit Gray code and converts it into 4bit binary code.                      | 13,K3,CO2 |

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

**12531**

13. a) Develop a binary counter using JK flip flops to count in the following sequences: 000, 001, 010, 011, 100, 101, 111, 000. 13, K3, CO3

**OR**

- b) Develop T flipflop using D flipflop and JK flipflop using D flipflop. 13, K3, CO3

14. a) Establish an asynchronous sequential circuit with 2 inputs X and Y and with one output Z. Whenever Y is 1, input X is transferred to Z. When Y is 0; the output does not change for any change in X. Use SR latch for implementation of the circuit. 13, K3, CO4

**OR**

- b) Develop asynchronous sequential circuit which is described by the following excitation and output function 13, K3, CO4

$$Y = X_1 X_2 + (X_1 + X_2) Y, Z = Y.$$

- (i) Draw the logic diagram of the circuit.
- (ii) Derive the transition table and output map and describe the behavior of the circuit.
15. a) (i) Explain the Race-free state assignment procedure. 7, K3, CO5
- (ii) Reduce the number of states in the following state diagram. Tabulated the reduced state table and Draw the reduced state diagram. 6, K3, CO5

Present state	Next state		output
	x=0	x=1	x=0, x=1
A	A	B	0,0
B	C	D	0,0
C	A	D	0,0
D	E	F	0,1
E	A	F	0,1
F	G	F	0,1
G	A	F	0,1

**OR**

- b) Develop a serial adder using a full adder and a flipflop. 13, K3, CO5

**PART - C (1 × 15 = 15 Marks)**

16. a) Implement the switching functions. 15, K3, CO6

$$Z1 = ab'd'e + a'b'c'd'e + bc + de;$$

$$Z2 = a'c'e; Z3 = bc + de + c'd'e + bd;$$

$$Z4 = a'c'e + \text{ceusing } 5 \times 8 \times 4 \text{ PLA}$$

**OR**

- b) Implement the following function using PAL. 15, K3, CO6
- $$F1(A, B, C) = \Sigma(1, 2, 4, 6);$$
- $$F2(A, B, C) = \Sigma(0, 1, 6, 7);$$
- $$F3(A, B, C) = \Sigma(1, 2, 3, 5, 7).$$