

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12682
---------------------	-------

M.E. / M.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024

Second Semester

M.E - Communication Systems

20PCOPC202 - MIC AND RF SYSTEM DESIGN

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

	<i>Marks</i>	<i>K- Level</i>	<i>CO</i>
1. Relate Direct up conversion and 2 step conversion.	2	K1	CO1
2. Show the formula to calculate sensitivity.	2	K1	CO1
3. Illustrate Q point and load line concepts.	2	K2	CO2
4. Define transducer gain of an amplifier.	2	K1	CO2
5. Contrast linear and non-linear mixer	2	K2	CO4
6. List out the basic characteristics of mixer.	2	K1	CO4
7. Summarize the steps in finding root locus	2	K2	CO5
8. Define ACPR Metric.	2	K1	CO5
9. What are the effects of nonlinearity in power amplifier?	2	K1	CO6
10. Classify power amplifier along with its performance parameters.	2	K2	CO6

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Describe the Thermal, Shot, Flicker, Popcorn noise and its effects on MOSFET.	13	K2	CO1
OR			
b) i) Illustrate Transceiver Specification distributed over a link.	5	K2	CO1
ii) Explain in detail about the direct up conversion and two step up conversion process.	8	K2	CO1
12. a) i) Name any three properties of S parameters and prove it.	5	K1	CO2
ii) Illustrate the significance of impedance matching in RF ICs with an example.	8	K2	CO2
OR			
b) Interpret Single ended and Differential LNAs and compare its Performance metrics.	13	K2	CO2

13. a) Explain the microwave components directional couplers, hybrid couplers and detectors. 13 K2 CO4

OR

b) i) How frequency multiplication and synthesis can be done by modifying the PLL? 5 K1 CO4

ii) Explain the various resonator configurations with neat diagrams. 8 K2 CO4

14. a) Explain in detail the types of efficiency boosting techniques in detail. 13 K2 CO5

OR

b) Identify and explain the following statements:- 7 K3 CO5

i) Negative feedback amplifier extends bandwidth. 6 K3 CO5

ii) Negative feedback reduces noise. 6 K3 CO5

15. a) Illustrate the principles of class E and F amplifiers with neat diagrams. 13 K2 CO6

OR

b) Derive efficiency of a class B power amplifier and explain. 13 K2 CO6

PART - C (1 × 15 = 15 Marks)

16. a) Explain Micro strip components and coplanar circuits in detail. 15 K2 CO3

OR

b) Explain in detail the selection of substrate material for MIC component fabrications. 15 K2 CO3