

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12368
---------------------	-------

M.E. / M.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023

First Semester

M.E.-Power Electronics and Drives

20PPEPC103 - ANALYSIS AND DESIGN OF POWER CONVERTERS

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

- | | <i>Marks,
K-Level, CO</i> |
|---|-------------------------------|
| 1. What is the inversion mode of converters? | <i>2,K1,CO1</i> |
| 2. What is meant by the non-circulating mode of operation of a dual converter? | <i>2,K1,CO1</i> |
| 3. Draw the sketch of Battery Charger? | <i>2,K1,CO2</i> |
| 4. List any two applications of SMPS. | <i>2,K1,CO2</i> |
| 5. Mention the soft magnetic materials. | <i>2,K1,CO3</i> |
| 6. Define the filling factor. | <i>2,K1,CO3</i> |
| 7. Define the term switching loss. | <i>2,K1,CO4</i> |
| 8. Draw the high-frequency equivalent circuit of zero- voltage transition PWM converters. | <i>2,K1,CO4</i> |
| 9. Define On - Off control of AC voltage regulators. | <i>2,K1,CO5</i> |
| 10. Define matrix converter. | <i>2,K1,CO5</i> |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Explain the operation of a single phase full bridge converter with R-L load for continuous and discontinuous load current. *13,K2,CO1*
- OR**
- b) Explain the pulse width modulation technique for power factor improvement. *13,K2,CO1*
12. a) Draw and explain the block diagram of SMPS and mention its advantages over linear power supply. *13,K2,CO2*
- OR**
- b) Discuss the basic operation of a Flyback converter showing various modes and draw the steady state waveforms of discontinuous mode operation. *13,K2,CO2*

13. a) Illustrate the optimum flux density unlimited by saturation in transformer design. *13,K2,CO3*

OR

- b) Analyze and design of methodology for inductor design. *13,K2,CO3*

14. a) Summarize the basic principles of soft switching and hard switching. *13,K2,CO4*

OR

- b) Explain in detail the Zero-Current Transition PWM Converters and sketch the waveforms. *13,K2,CO4*

15. a) (i) Derive the RMS output voltage for a single phase half controlled ac voltage controller with R-load. *7,K2,CO5*

- (ii) Draw the voltage and current waveform with R load and R-L load and justify the shape of the waveform. *6,K2,CO5*

OR

- b) Explain with circuit diagram and waveform the principle of phase control of single phase controller with RL load and obtain expression for voltage and power factor. *13,K2,CO5*

PART - C (1 × 15 = 15 Marks)

16. a) Explain the working of SEPIC Converter in detail with necessary waveforms and equations. *15,K2,CO2*

OR

- b) Design a transformer single-capacitor phase-controlled series-resonant converter with a transformer center - tapped rectifier. The specifications are $V_I = 270$ to 300 V, $V_O = 28$ V, and $R_{L_{min}} = 10 \Omega$. Assume the resonant frequency $f_0 = 150$ kHz, the inverter efficiency $\eta_I = 94\%$, and the rectifier efficiency $\eta_R = 95\%$. Draw the efficiency of the designed converter η as a function of load resistance RL. *15,K2,CO4*