



- b) i) Evaluate the fly back converter and draw the steady state waveforms of discontinuous mode operation. 10 K3 CO2  
 ii) Compare fly back converter with forward converter. 3 K3 CO2
13. a) Design an inductor for a buck converter with suitable specifications. 13 K3 CO3  
**OR**  
 b) Evaluate the selection of input and output filter capacitors. 13 K3 CO3
14. a) Summarize the operation of series loaded resonant converter and parallel loaded resonant converter with suitable sketches and waveform. 13 K2 CO4  
**OR**  
 b) Evaluate the Buck-Boost ZCS Quasi Resonant DC-DC Converter with its suitable circuit and characteristics. 13 K2 CO4
15. a) Elucidate with circuit diagram and waveform the principle of phase control of single phase controller with RL load and obtain expression for voltage and power factor. 13 K2 CO5  
**OR**  
 b) Illustrate the operating principle of three phase to single phase cycloconverter with appropriate circuit and waveform. 13 K2 CO5
- PART - C (1 × 15 = 15 Marks)**
16. a) With neat sketches, explicate the operation of single phase dual converter in circulating current mode with its suitable waveform. 15 K5 CO1  
**OR**  
 b) Illustrate three phase to three phase cyclo converter with relevant circuit arrangements. Draw and explain the control circuit block diagram for a cyclo converter with non- circulating current mode. 15 K4 CO5