

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12817
---------------------	-------

M.E. / M.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024

First Semester

M.E - Power Electronics and Drives

20PPEPC104 - ANALYSIS AND DESIGN OF INVERTERS

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

	Marks	K- Level	CO
1. Define commutation. How they are generally classified?.	2	K1	CO1
2. Why IGBT is preferred for inverters?	2	K1	CO1
3. Define amplitude and frequency modulation index.	2	K1	CO2
4. Define PWM inverter	2	K1	CO2
5. What is a six step thyristor Inverter?	2	K1	CO3
6. What are the advantages of CSI when compared to VSI ?	2	K1	CO3
7. Mention the disadvantages of a modified diode-clamped multilevel inverter.	2	K1	CO4
8. List out the advantages and disadvantages of cascaded inverters.	2	K1	CO4
9. What are the advantages of resonant inverters?	2	K1	CO5
10. Mention the advantages and limitations of class E resonant inverter.	2	K1	CO5

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) Describe the operation of half phase full bridge inverter with RL Load and derive the expression for fundamental component of RMS output voltage.	13	K2	CO1
--	----	----	-----

**OR**

b) Explain the modified Mc-Murray full bridge inverter with appropriate voltage and current waveforms. Derive suitable expressions for commutating components of L and C.	13	K2	CO1
12. a) Explain the principle of operation of three phase operating at 180° conduction mode with star connected load, with neat waveforms and circuit diagram.	13	K2	CO2

**OR**

b) A 3φ bridge inverter delivers power to a resistive load from a 450V dc source. For a star connected load of 10Ω/phase, determine for both 180° and 120° mode operation. (i) RMS value of load current. (ii) RMS value of thyristor current. (iii) Load power.	13	K2	CO2
---	----	----	-----

13. a) Explain the operation of three phase auto sequentially commutated current source inverter in detail. 13 K2 CO3

**OR**

- b) A single phase bridge inverter fed from 230V dc is connected to RL load with  $R= 20 \text{ Ohm}$  and  $L= 0.06\text{H}$ . Determine power delivered to load in case inverter is operating at 50Hz with  
(i) Square wave output.  
(ii) Quasi square wave output with on period of 0.5  
Two Symmetrically spaced pulses per half cycle on period of 0.5 of cycle. 13 K2 CO3

14. a) Explain the different waveforms of diode-clamped multilevel inverter with necessary equations. 13 K2 CO4

**OR**

- b) Explain the operation of a flying capacitor multilevel inverter with necessary details and also discuss its features, advantages and disadvantages. 13 K2 CO4

15. a) Describe the operation of Class E resonant inverter with neat wave forms. 13 K2 CO5

**OR**

- b) Explain the step by step procedure for the design of zero-voltage switching resonant converter. 13 K2 CO5

**PART - C (1 × 15 = 15 Marks)**

16. a) Discuss in detail the different PWM techniques used for single phase multilevel inverters. 15 K2 CO4

**OR**

- b) Explain the principle of series resonant inverter. 15 K2 CO5