



15.	Distinguish between PNP and NPN transistors.	2	K2	CO3
16.	What is the working principle of JFET?	2	K1	CO3
17.	What are the conditions for positive feedback?	2	K1	CO4
18.	Define bandwidth of an amplifier.	2	K1	CO4
19.	Draw the schematic symbol of an operational amplifier indicating the various terminals.	2	K1	CO5
20.	What is voltage follower?	2	K1	CO5
21.	Difference between Half adder and Full adder.	2	K2	CO6
22.	Mention any two applications of multiplexers.	2	K1	CO6

**PART - C (6 × 11 = 66 Marks)**

Answer ALL Questions

23.	a) Apply the intrinsic carrier concentration relationship to describe how the balance between electrons and holes changes when the semiconductor is doped.	11	K3	CO1
	<b>OR</b>			
	b) Apply the concept of carrier concentration in a N-type semiconductor to describe how the electrical properties of a semiconductor device change with temperature.	11	K3	CO1
24.	a) Explain the process of biasing and current flow in a PN junction diode.	11	K2	CO2
	<b>OR</b>			
	b) Explain the construction and working of a full-wave rectifier with a suitable circuit diagram and waveform.	11	K2	CO2
25.	a) Identify the characteristics of a transistor in C-B configuration and discuss how transistor parameters can be evaluated.	11	K2	CO3
	<b>OR</b>			
	b) Explain the working principles of an n-JFET to analyze its behavior during ON and OFF states in a switching circuit.	11	K2	CO3
26.	a) Construct a Hartley oscillator circuit and explain how its components determine the frequency and amplitude of oscillation.	11	K2	CO4
	<b>OR</b>			
	b) In designing a feedback control system for a precision amplifier, how would you utilize VCVS and CCVS configurations to optimize the system's performance? Discuss.	11	K2	CO4
27.	a) Describe the construction of differentiator circuit in op-amp and explain how the output voltage represents the derivative of the input signal.	11	K2	CO5
	<b>OR</b>			
	b) Apply your knowledge of the non-inverting op-amp configuration to construct a circuit that achieves a specified voltage gain and explain how the resistor values determine the gain.	11	K2	CO5
28.	a) Develop a de-multiplexer-based circuit to route a single input signal to multiple outputs and explain its working and functions with necessary diagrams.	11	K3	CO6
	<b>OR</b>			
	b) Reduce the following Boolean expression: $A = XY + X(Y+Z) + Y(Y+Z)$ .	11	K3	CO6