

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2025

Third Semester

Electrical and Electronics Engineering
24EPC303 - ANALOG ELECTRONICS

Regulations - 2024

Duration: 3 Hours

Max. Marks: 100

PART - A (MCQ) (10 × 1 = 10 Marks)

Answer ALL Questions

	<i>Marks</i>	<i>K- Level</i>	<i>CO</i>
1. The CMRR of an ideal differential amplifier is ____. (a) infinite (b) zero-bias (c) positive (d) negative	1	K1	CO1
2. _____ is the most common type of JFET biasing. (a) Self biasing (b) Voltage biasing (c) Current biasing (d) All of the mentioned	1	K1	CO1
3. The Q point of Class B is in _____. (a) Cut-off region (b) saturation region (c) active region (d) breakdown region	1	K1	CO2
4. Crossover distortion behavior is characteristic of _____ Power amplifier. (a) Class A (b) Class AB (c) Class B (d) None of the mentioned	1	K1	CO2
5. The phase shift oscillator requires at least how many RC sections? (a) 1 (b) 2 (c) 3 (d) 4	1	K1	CO3
6. A Clapp oscillator is an improved version of: (a) Hartley oscillator (b) Colpitts oscillator (c) Wien bridge oscillator (d) Crystal oscillator	1	K1	CO3
7. Which op-amp configuration provides unity gain? (a) Inverting amplifier (b) Non-inverting amplifier (c) Voltage follower (d) Differentiator	1	K1	CO4
8. The input impedance of an ideal op-amp is: (a) Zero (b) High (in the range of kΩ) (c) Infinite (d) Very low	1	K1	CO4
9. A sample-and-hold circuit is essential in ADCs because: (a) ADCs take finite conversion time (b) It reduces noise (c) It increases resolution (d) It eliminates need for DAC	1	K1	CO5
10. In Monostable mode, the output pulse width of 555 timer depends on: (a) Only capacitor (b) Only resistor (c) Both resistor and capacitor (d) Supply voltage	1	K1	CO6

PART - B (12 × 2 = 24 Marks)

Answer ALL Questions

11. Compare BJT and FET.	2	K2	CO1
12. Draw the circuit for Dual Input Unbalanced Output.	2	K1	CO1
13. Define negative feedback.	2	K1	CO2
14. Compare class A and class B amplifier.	2	K2	CO2
15. Define barkhausen criteria.	2	K1	CO3
16. Compare oscillator and amplifier.	2	K2	CO3
17. List the important characteristics of an ideal operational amplifier.	2	K1	CO4
18. Draw the circuit diagram of an op-amp differentiator.	2	K1	CO4
19. Define sample and hold period of S/H circuit.	2	K1	CO5
20. Classify the ADC converters.	2	K2	CO5
21. List any two advantages of switching regulators when compared to linear regulators.	2	K1	CO6
22. Define line and load regulation.	2	K1	CO6

PART - C (6 × 11 = 66 Marks)

Answer ALL Questions

23. a) Analyze the concept of stability in Voltage divider network using BJT and comment the stability against β variations. 11 K3 CO1
- OR**
- b) Construct the circuit diagram of a differential amplifier and list its various configurations with common mode gain and differential mode gain to derive CMRR. 11 K3 CO1
24. a) Apply the concept of Q point in Class-A Amplifier and derive the conversion efficiency. 11 K3 CO2
- OR**
- b) Construct the ClassAB push-pull power amplifier based on the conduction Q point and justify how the crossover distortion is eliminated. Also list the merits and demerits. 11 K3 CO2
25. a) Apply the concept of barkhausen criteria in wein bridge oscillator and derive the expression for the frequency of oscillation. 11 K2 CO3
- OR**
- b) Describe the construction and working of a Colpitts oscillator. Derive the expression for oscillation frequency and discuss its key characteristics. 11 K2 CO3
26. a) Explain the AC performance characteristics of an operational amplifier in detail. 11 K3 CO4
- OR**
- b) Construct the diagram for inverting and non inverting summing amplifier using OP-AMP and derive the output voltage. 11 K3 CO4
27. a) Analyze the operation of an instrumentation amplifier with a neat diagram 11 K4 CO5
- OR**
- b) Analyze the principle of operation of a Successive Approximation ADC with a neat diagram. 11 K4 CO5
28. a) With a neat diagram, explain the functional block diagram of a 555-timer-based Monostable multivibrator and apply the timing principles to derive the expression for its time delay. 11 K2 CO6
- OR**
- b) Explain the operation of fixed voltage regulators with the help of block diagrams. Apply the concepts to identify their typical applications. 11 K2 CO6