

B.E. / B.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2025

Third Semester

Computer Science and Engineering (IoT)

24ESCI301 - BASIC ELECTRONICS AND COMMUNICATION ENGINEERING

Regulations - 2024

Duration: 3 Hours

Max. Marks: 100

PART - A (MCQ) (10 × 1 = 10 Marks)


Answer ALL Questions

- | | Marks | K-
Level | CO |
|---|-------|-------------|-----|
| 1. In a node basis matrix equation, node voltages are solved by using _____.
(a) Cramer's rule (b) Matrix Inversion
(c) Gaussian Elimination (d) Successive Over-Relaxation | 1 | K1 | CO1 |
| 2. When n number of identical resistances of value R are connected in parallel, the equivalent value of the parallel combination is,
(a) nR (b) R/n (c) 2R/n (d) R/2n | 1 | K1 | CO1 |
| 3. Which transistor configuration provides the highest current gain?
(a) Common-base (b) Common-emitter
(c) Common-collector (d) All provide equal gain | 1 | K1 | CO2 |
| 4. Biasing is required to keep the transistor in
(a) Active region (b) Saturation (c) Cutoff (d) Breakdown | 1 | K1 | CO2 |
| 5. In an inverting amplifier using an op-amp, the concept of _____ is applied at the inverting input terminal.
(a) Ground (b) virtual ground (c) +Vcc (d) -Vcc | 1 | K1 | CO3 |
| 6. The _____ of an op-amp is the ratio of output voltage change to time
(a) Voltage bias (b) current bias (c) slew rate (d) off set null | 1 | K1 | CO3 |
| 7. Entropy gives
(a) Amount of information (b) Rate of information
(c) Measure of uncertainty (d) probability of message | 1 | K1 | CO4 |
| 8. Mutual information is given by:
(a) $I(X;Y) = H(X) - H(X Y)$ (b) $I(X;Y) = H(X) + H(Y)$
(c) $I(X;Y) = H(X,Y) - H(X)$ (d) $I(X;Y) = H(X,Y) + H(Y)$ | 1 | K1 | CO4 |
| 9. FM modulation index is
(a) $\Delta f / f_m$ (b) $f_m / \Delta f$ (c) $\Delta f / f_c$ (d) $f_c / \Delta f$ | 1 | K1 | CO5 |
| 10. Aliasing occurs when the sampling rate is
(a) Less than Nyquist rate (b) Equal to Nyquist rate
(c) More than Nyquist rate (d) Infinite | 1 | K1 | CO6 |

PART - B (12 × 2 = 24 Marks)

Answer ALL Questions

- | | | | |
|--|---|----|-----|
| 11. Solve for the current flowing through 8Ω resistor. | 2 | K2 | CO1 |
|--|---|----|-----|

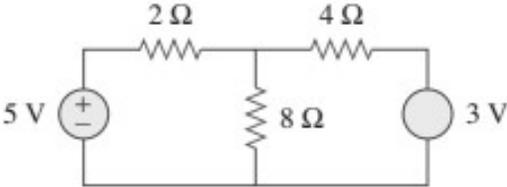


- | | | | |
|--|---|----|-----|
| 12. State maximum power transfer theorem. | 2 | K1 | CO1 |
| 13. What is "Thermal runaway" in transistors and mention how it can be avoided? | 2 | K1 | CO2 |
| 14. Differentiate between zener breakdown and avalanche breakdown. | 2 | K2 | CO2 |
| 15. Assuming a slew rate for 741 IC is 0.5v/ μs. What is the maximum undistorted sine wave that can be obtained for 12 V peak. | 2 | K2 | CO3 |
| 16. Define Shannon's Channel Capacity theorem. | 2 | K1 | CO3 |

- | | | | |
|---|---|----|-----|
| 17. List the properties Entropy. | 2 | K1 | CO4 |
| 18. What is the pre-emphasis and de-emphasis? | 2 | K1 | CO4 |
| 19. Write the formulae for calculating modulation index for AM and FM signal. | 2 | K1 | CO5 |
| 20. Recall the steps in pulse code modulation. | 2 | K1 | CO5 |
| 21. Draw the BPSK signal for the given input bit stream 101010. | 2 | K1 | CO6 |
| 22. Compare TDM with FDM. | 2 | K2 | CO6 |

PART - C (6 × 11 = 66 Marks)

Answer ALL Questions

- | | | | | |
|--------|---|----|----|-----|
| 23. a) | Determine the currents in various elements of the bridge circuit shown in Fig. using mesh analysis. | 11 | K3 | CO1 |
|--------|---|----|----|-----|

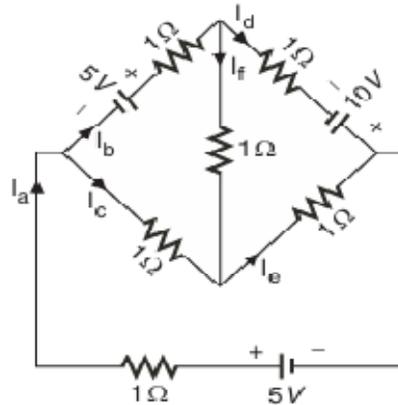

OR

- | | | | | |
|--------|--|----|----|-----|
| b) | A source has $V_{th} = 30\text{ V}$ and $R_{th} = 10\ \Omega$. It supplies a variable load R_L .
(i) Find the value of R_L for maximum power transfer.
(ii) Calculate the maximum power delivered to the load.
(iii) Plot the relationship between load power and load resistance. | 11 | K3 | CO1 |
| 24. a) | Summarize the input and output characteristics of a transistor in CE configuration. | 11 | K2 | CO2 |
| | OR | | | |
| b) | Explain the construction, working and characteristics of a PN junction diode with suitable diagrams and graph. | 11 | K2 | CO2 |
| 25. a) | Explain Instrumentation Amplifier using Op-Amps for amplifying a sensor signal and derive the gain equation. | 11 | K2 | CO3 |
| | OR | | | |
| b) | Illustrate the working of differentiator and integrator using IC741. | 11 | K2 | CO3 |
| 26. a) | A source emits symbols A, B, C, D with probabilities 0.5, 0.25, 0.15, and 0.10. Compute the entropy of the source. | 11 | K3 | CO4 |
| | OR | | | |
| b) | For a source X with probabilities (0.5, 0.3, 0.2) and a channel where $H(Y X)=0.4$ bits. Calculate:(a) $H(X)$, (b) $H(Y)$, (c) $I(X;Y)$. | 11 | K3 | CO4 |
| 27. a) | Explain the generation of SSB by Phase shift method and also derive the equation. | 11 | K2 | CO5 |
| | OR | | | |
| b) | Interpret the working of Pulse Code Modulation system with a block diagram. | 11 | K2 | CO5 |
| 28. a) | Compare ASK, FSK and PSK in terms of bandwidth efficiency, power requirement and robustness against noise. | 11 | K2 | CO6 |
| | OR | | | |
| b) | Illustrate in detail about ground wave and space wave propagation. | 11 | K2 | CO6 |