



20. Compare and contrast the key difference between Function generator and Sine wave Generator. 2 K3 CO5
21. Mention the two advantages of XY recorders. 2 K1 CO6
22. Choose a suitable display for showing alphanumeric data on a portable device and State why? 2 K2 CO6

**PART - C (6 × 11 = 66 Marks)**

Answer ALL Questions

23. a) Interpret how MI instruments can be used for both AC and DC measurement using construction diagrams with different vane arrangements. Interpret why MI instruments cannot be accurate for DC measurement. 11 K3 CO1

**OR**

- b) Develop the torque equation for a PMMC instrument. Show that its scale is linear if spring control is employed and list out the advantages. 11 K3 CO1

24. a) (i) A Maxwell's capacitance bridge is used to measure an unknown Inductance in comparison with capacitance.  $R_2 = 200 \Omega$ ,  $R_3 = 300 \Omega$ ,  $R_4 = 500 \Omega$ ,  $C_4 = 0.25 \mu\text{F}$ . Calculate the values of  $R_1$  and  $L_1$ . 6 K3 CO2

- (ii) Describe the different difficulties encountered in the measurement of high resistances. 5 K2 CO2

**OR**

- b) (i) In a Wheatstone bridge circuit, the four arms have the following resistances: Arm AB =  $100 \Omega$ , Arm BC =  $200 \Omega$ , Arm CD =  $150 \Omega$ , Arm DA = R (unknown). A galvanometer is connected between points B and D, and the bridge is balanced when the resistances are connected as above. Compute the value of the unknown resistance R. 6 K3 CO2

- (ii) Discuss how the Schering bridge is used for the measurement of capacitance with a neat diagram. 5 K3 CO2

25. a) Illustrate the working of Precision – Crompton's DC potentiometer and with neat sketch. Describe the steps used when measuring an unknown resistance. 11 K2 CO3

**OR**

- b) Explain the Potential Transformer with principle, construction and working in detail. 11 K2 CO3

26. a) Summarize the working and construction of basic wave analyzer and Heterodyne wave analyzer type. 11 K2 CO4

**OR**

- b) With neat sketch enumerate the working and construction of Successive Approximate Register DVM. 11 K2 CO4

27. a) Construct with a neat diagram the block diagram and working principle of a Dual beam and Dual trace Cathode Ray Oscilloscope (CRO). 11 K3 CO5

**OR**

- b) Illustrate with neat sketch the operation of Square Wave and AF Sine Wave Generators with diagrams. 11 K3 CO5

28. a) Describe the construction and operation of a Seven Segment Display. Give its types and typical applications. 11 K3 CO6

**OR**

- b) Discuss the factors influencing the selection of display and recording devices for a given instrumentation application. 11 K3 CO6