

Reg. No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	13335
---------------------	-------

M.E. / M.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2024 (JAN – 2025)

First Semester

M.E. - Embedded Systems Technologies

24PESPC101 - ADVANCED DIGITAL PRINCIPLES AND DESIGN

Regulations - 2024

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)


Answer ALL Questions

- | | Marks | K-Level | CO |
|---|-------|---------|-----|
| 1. Give the excitation table for JK flipflop. | 2 | K1 | CO1 |
| 2. What is the important component in ASM chart for the asynchronous design? | 2 | K1 | CO1 |
| 3. List the rules for state assignment. | 2 | K1 | CO2 |
| 4. Compare synchronous and asynchronous circuits. | 2 | K2 | CO2 |
| 5. Name some of the algorithms used to reduce the time complexity in fault diagnosis. | 2 | K1 | CO3 |
| 6. Show the importance of test set and their types. | 2 | K2 | CO3 |
| 7. What are the advantages of reconfigurable logic designs? | 2 | K1 | CO4 |
| 8. Define interconnects and mention its types. | 2 | K1 | CO4 |
| 9. Interpret the significance of component definition. | 2 | K2 | CO5 |
| 10. List the different VHDL modeling. | 2 | K1 | CO5 |

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

 11. a) Construct the following synchronous sequential circuit and give the Transition table, Excitation table, state table and state diagram. 13 K2 CO1



OR

- b) An Asynchronous sequential circuit is given by the following excitation and output function 13 K2 CO1
- $$Y = X_1X_2 + (X_1+X_2)Y$$
- $$Z = Y$$
- Draw the logic diagram of the circuit.
Derive the transition table and output map.

12. a) For the state table of a asynchronous circuit identify the stable states and draw the flow diagram. 13 K2 CO2


Present state	Next state				Output z			
	Inputs $x_1 x_2$				Inputs $x_1 x_2$			
	00	01	10	11	00	01	10	11
A	A	C	A	B	0	0	0	0
B	A	A	B	B	0	0	1	0
C	C	C	D	B	1	0	1	0
D	C	D	D	B	1	1	1	0

OR

- b) Construct the ASM chart for Mod-8 binary counter. 13 K2 CO2
13. a) Explain in detail the different types of faults and the steps involved in fault diagnosis. 13 K2 CO3

OR

 - b) Identify the static hazard in the below circuit given and also eliminate the same. 13 K2 CO3



14. a) Explain in detail the Xilinx 4000 Architecture in detail with necessary diagram. 13 K2 CO4

OR

- b) Explain in detail the Input output block of Xilinx 2000. 13 K2 CO4

15. a) A combinational logic circuit is defined by the function given below. Implement the circuit using Programmable logic Array. 13 K2 CO5

$$F(A,B,C,D) = \sum m(3,4,5,7,10,14,15)$$

$$G(A, B, C, D) = \sum (3,4,5,7,10,14,15)$$

OR

- b) Construct the following four Boolean functions using PAL. 13 K2 CO5

$$F1(W,X,Y,Z) = \sum m(0,1,2,3,7,9,11)$$

$$F2(W,X,Y,Z) = \sum m(0,1,2,3,10,12,14)$$

$$F3(W,X,Y,Z) = \sum m(0,1,2,3,10,13,15)$$

$$F4(W,X,Y,Z) = \sum m(4,5,6,7,9,15)$$

PART - C (1 × 15 = 15 Marks)

16. a) Explain in detail the VHDL code for Ripple carry Adder. 15 K2 CO6

OR

- b) Explain in detail the logic design flow of VHDL. 15 K2 CO6