



21. Differentiate between hard switching and soft switching. 2 K2 CO4  
 22. Mention two applications of AC voltage controllers. 2 K2 CO5

**PART - C (6 × 11 = 66 Marks)**

Answer ALL Questions

23. a) Construct the single-phase dual converter with necessary circuit diagram and waveforms. 11 K3 CO1

**OR**

- b) Construct the single phase full converter operation with RLE load. Draw relevant waveforms and derive the output voltage equation. 11 K3 CO1

24. a) Construct the Boost converter and explain its operation with circuit diagram showing the various modes. 11 K3 CO2

**OR**

- b) Construct the Flyback converter showing various modes and draw the steady state waveforms of discontinuous mode operation. 11 K3 CO2

25. a) Explain the design steps of a transformer used in power converters with relevant equations. 11 K2 CO3

**OR**

- b) Explain the design procedure of an inductor for a buck/flyback converter with suitable specifications. 11 K2 CO3

26. a) Summarize the basic principles of soft switching. 11 K2 CO4

**OR**

- b) Summarize the operation of Zero Current Switching (ZCS) and Zero Voltage Switching (ZVS). 11 K2 CO4

27. a) Explain in detail the principle of on-off and phase angle control in AC voltage controllers. 11 K2 CO5

**OR**

- b) With a detailed note on matrix converters, explain their working principles and advantages. 11 K2 CO5

28. a) A 3 phase bridge converter is used for obtaining a regulated DC output voltage. The supply voltage is 440V and the firing angle is maintained at  $60^\circ$  so that the load current is 15 A; Calculate the DC output voltage, active and reactive power input. 11 K3 CO1

**OR**

- b) A six pulse thyristor converter connected on the secondary of delta /star connected 6.6 kV /415V, 50 Hz transformer is supplying to 460 V, 200 A DC load. Identify the converter firing angle, dc power delivered by the converter and AC line current. 11 K3 CO1