



**OR**

- b) Illustrate the Push-pull converter configuration and Derive the expression for average output voltage. 13 K2 CO2

13. a) Interpret the selection of output capacitor. 13 K3 CO3

**OR**

- b) Identify the core loss and describe the optimum effective Permeability in inductor design. 13 K3 CO3

14. a) Compare the Zero Current Switching (ZCS)/ Zero Voltage Switching (ZVS). 13 K2 CO4

**OR**

- b) Summarize the classification of resonant converters. 13 K2 CO4

15. a) Develop the expression for RMS output voltage, RMS load current and RMS thyristor current of a single phase full wave AC voltage controller for RL load. 13 K3 CO5

**OR**

- b) Explain the operation of a 3phase AC voltage regulator having six thyristors with neat sketches of voltage waveforms. Derive the expression for the RMS output voltage, RMS load current and RMS thyristor current for a single phase full wave AC voltage controller for R load. 13 K3 CO5

**PART - C (1× 15 = 15 Marks)**

16. a) The single phase dual converter is operated from a 120V, 60 Hz supply and the load resistance is  $R=10\Omega$ . The circulating inductance is  $L_r=40\text{mH}$ . delay angles are  $\alpha_1=60^\circ$  and  $\alpha_2=120^\circ$ . Design the peak circulating current and peak current of converter. 15 K2 CO1

**OR**

- b) Summarize the Three phase operation of semi-converter R and RL load and Evaluate the power factor improvement techniques and explain the reactive power. 15 K2 CO1