

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	14213
---------------------	-------

**M.E. / M.Tech - DEGREE EXAMINATIONS, NOV / DEC 2025**

First Semester

**M.E. - Power Electronics and Drives**

**24PPEPC104 - ANALYSIS AND DESIGN OF INVERTERS**

Regulations - 2024

Duration: 3 Hours

Max. Marks: 100

**PART - A (MCQ) (10 × 1 = 10 Marks)**

Answer ALL Questions

	Marks	K- Level	CO
1. The output of a single-phase half-bridge inverter on an R load is ideally: (a) a sine wave      (b) a square wave      (c) a triangular wave      (d) a constant dc	1	K1	CO1
2. In a single-phase full bridge inverter, how many SCR(s) are gated at a time? (a) One      (b) Two      (c) Three      (d) None of the mentioned	1	K1	CO1
3. In case of the 120° mode of operation, _____ devices conduct at a time. (a) 2      (b) 3      (c) 4      (d) none of the mentioned	1	K1	CO2
4. If T1 is gated at 0°, T3 and T5 will start conducting at _____ and _____ respectively. (a) 180°, 270°      (b) 120°, 240°      (c) 180°, 300°      (d) 240°, 360°	1	K1	CO2
5. Force-commutated CSIs need (a) capacitors for their commutation      (b) inductors for their commutation (c) diodes for their commutation      (d) none of the mentioned	1	K1	CO3
6. In current source inverters (CSIs), the output voltage's (a) amplitude depends upon the load impedance (b) waveform depends upon the load impedance (c) amplitude as well as the nature of the waveform depends on the load (d) both amplitude and waveform are independent of the load impedance	1	K1	CO3
7. Which of the following is NOT a type of multilevel inverter? (a) Diode Clamped Multilevel Inverter      (b) Balancing Capacitor Multilevel Inverter (c) Cascaded H-Bridge Multilevel Inverter      (d) Cycloconverter	1	K1	CO4
8. What is a key characteristic of the output voltage waveform of a multilevel inverter? (a) It is similar to a square wave (b) It has a lower total harmonic distortion (THD) (c) It consists of a single high-amplitude pulse (d) It is used only for high-frequency applications	1	K1	CO4
9. Which of the following is an advantage of using a resonant inverter? (a) Higher switching losses compared to conventional inverters (b) Increased harmonic distortion in the output waveform (c) Controlled commutations that make semiconductor device control easier (d) A smaller physical size for a given power rating	1	K1	CO5
10. What is a key characteristic of the load in a resonant inverter? (a) The load must be a purely resistive element (b) The load must be a slightly damped oscillating circuit (c) The load must be a constant current source (d) The load must be able to handle extremely high switching frequencies	1	K1	CO5

**PART - B (12 × 2 = 24 Marks)**

Answer ALL Questions

11. Discuss the purpose of connecting diodes in antiparallel with thyristor in inverter Circuit.	2	K1	CO1
12. State the need of commutation circuit in forced commutated inverters.	2	K1	CO1
13. Mention the advantages of voltage control by PWM methods.	2	K1	CO2

*K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create*

**14213**

- |  |   |    |     |
|--|---|----|-----|
| 14. Distinguish 180 and 120 degree modes of operation.                         | 2 | K2 | CO2 |
| 15. Define load commutated inverter.   | 2 | K1 | CO3 |
| 16. Draw the circuit of ASCI with series R-L load.                             | 2 | K1 | CO3 |
| 17. What are the features of cascaded inverter?                                | 2 | K1 | CO4 |
| 18. What is meant by two level inverter?                                       | 2 | K1 | CO4 |
| 19. Define dead zone of a resonant converter.                                  | 2 | K1 | CO5 |
| 20. How the output voltage is controlled in series resonant inverters?         | 2 | K1 | CO5 |
| 21. List the advantages and disadvantages of a flying capacitor.               | 2 | K1 | CO4 |
| 22. What is the purpose of coupled inductor in half-bridge resonant inverters? | 2 | K1 | CO5 |

**PART - C (6 × 11 = 66 Marks)**

Answer ALL Questions

- |   |    |    |     |
|---|----|----|-----|
| 23. a) Outline the operation of half bridge VSI and obtain the steady state analysis for RL load.             | 11 | K2 | CO1 |
| <b>OR</b>   |    |    |     |
| b) Explain different voltage control techniques.  | 11 | K2 | CO1 |
| 24. a) Discuss in detail about Space Vector Modulation.   | 11 | K2 | CO2 |
| <b>OR</b>   |    |    |     |
| b) Explain the operation of 3 phase VSI feeding star load in 120 degree mode.                                 | 11 | K2 | CO2 |
| 25. a) Interpret the operation of three phase auto sequentially commutated current source inverter in detail. | 11 | K2 | CO3 |
| <b>OR</b>   |    |    |     |
| b) Explain the operation of any one load commutated inverter in detail.                                       | 11 | K2 | CO3 |
| 26. a) Illustrate the different PWM techniques used in MLI.   | 11 | K2 | CO4 |
| <b>OR</b>   |    |    |     |
| b) Summarize the operation of diode clamped multilevel inverter with necessary diagrams and waveforms.        | 11 | K2 | CO4 |
| 27. a) Describe the operation of Class E resonant inverter with neat wave forms.                              | 11 | K2 | CO5 |
| <b>OR</b>   |    |    |     |
| b) Summarize the procedure for the construction of series resonant converters.                                | 11 | K2 | CO5 |
| 28. a) (i) Draw the circuit and output voltage of 5-level CHB inverter and name the different elements.       | 5  | K2 | CO4 |
| (ii) Explain briefly the zero-current switching.  | 6  | K2 | CO5 |
| <b>OR</b>   |    |    |     |
| (b) (i) Illustrate the APOD PWM technique of MLI.   | 6  | K2 | CO4 |
| (ii) Explain about the power line disturbances.   | 5  | K2 | CO5 |