

Reg. No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	13371
---------------------	-------

**M.E. / M.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2024 (JAN - 2025)**

First Semester

**M.E. - Power Electronics and Drives**

**24PPEPC104 - ANALYSIS AND DESIGN OF INVERTERS**

Regulations - 2024

Duration: 3 Hours

Max. Marks: 100

**PART - A (10 × 2 = 20 Marks)**

Answer ALL Questions

	Marks	K- Level	CO
1. What should be the pulse width for the elimination of 3rd harmonic in the output voltage waveform of single phase inverter?	2	K1	CO1
2. Draw the waveform of single pulse-width modulation.	2	K1	CO1
3. Compare 120 degree mode with 180 degree mode operation of a three phase inverter.	2	K2	CO2
4. Define the space vector modulation for three phase inverter.	2	K1	CO2
5. State the reason why low power devices cannot be used in a CSI.	2	K1	CO3
6. Draw the ASCII voltage and current waveform.	2	K1	CO3
7. In an m-level diode clamped inverter how many main switching devices and clamping diodes are present?	2	K1	CO4
8. Plot the output waveform of five-level flying capacitor of single phase inverter.	2	K1	CO4
9. Write the necessary condition for series resonant oscillation.	2	K1	CO5
10. List the advantages of ZVS resonant converter.	2	K1	CO5

**PART - B (5 × 13 = 65 Marks)**

Answer ALL Questions

11. a) A single phase bridge inverter has a resistive load $R=2.4$ ohm and the DC input voltage of 48 V. determine a) RMS output voltage at fundamental frequency. b) Output power c) $I_{av}$ and $I_m$ of each transistor d) Peak reverse blocking voltage of each transistor e) HF and DF at the LOH.	13	K2	CO1
<b>OR</b>			
b) Enumerate the operation of half bridge VSI and obtain the steady state analysis for RL load.	13	K2	CO1
12. a) Suggest a suitable harmonic elimination technique to reduce the Total Harmonic Distortion factor of three phase inverter.	13	K2	CO2

**OR**

*K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create*

**13371**

b) Derive the fundamental voltage and current equations of three phase voltage source inverter fed star connected load for 120 degree mode of conduction. 13 K2 CO2

13. a) A star connected load of 25 ohm/phase is fed from 600V dc through a three phase bridge inverter per both 180 and 120 mode. Determine  
a. RMS value of load current  
b. RMS value of thyristor Current  
c. Load power. 13 K2 CO3

**OR**

b) Explain the operation of a six step current source inverter with inductive load. 13 K2 CO3

14. a) Explain the operation of flying capacitor multilevel inverter with necessary details. Also discuss its features advantages and disadvantages. 13 K2 CO4

**OR**

b) Enumerate application of multilevel converter connected to a power system for reactive power compensation. 13 K2 CO4

15. a) Analyze the step by step procedure for the design of zero-current switching resonant converter. 13 K3 CO5

**OR**

b) Develop the operation of Class E resonant inverter. 13 K3 CO5

**PART - C (1 × 15 = 15 Marks)**

16. a) A single phase bridge inverter fed from 230V dc is connected to load  $R=20$  ohm &  $L=0.06H$ . Determine power delivered to load in case inverter is operating at 50 Hz with (a) square wave output. (b) Quasi square wave output with on period of 0.5 (c) Two symmetrically spaced pulses per half cycle on period of 0.5 of cycle. 15 K2 CO3

**OR**

b) Outline the operation of online and offline UPS. 15 K2 CO5