

Reg. No.

Question Paper Code

13666

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2025

Third Semester

Computer and Communication Engineering

20CCPC301 - DIGITAL LOGICS AND SYSTEM DESIGN

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (MCQ) (10 × 1 = 10 Marks)**

Answer ALL Questions

- |  | Marks | K-Level | CO  |
|--|-------|---------|-----|
| 1. Which binary code is also known as the "8421 code"?<br>(a) Gray code      (b) Excess-3 code      (c) BCD      (d) 2's Complement  | 1     | K1      | CO1 |
| 2. The components used in the transistor are _____.<br>(a) Resistor      (b) Transistor      (c) Diode      (d) All of the mentioned   | 1     | K1      | CO1 |
| 3. The number of Boolean function which can be generated with four variable is<br>(a) 4      (b) 16      (c) 256      (d) 65536  | 1     | K1      | CO2 |
| 4. In a "Half Adder", the number of inputs is _____ and the number of outputs is _____.<br>(a) 2,1      (b) 2,2      (c) 3,1      (d) 1,2  | 1     | K1      | CO2 |
| 5. D flip flop is used as<br>(a) Differentiator      (b) Divider circuit<br>(c) Delay switch      (d) All of the mentioned   | 1     | K1      | CO3 |
| 6. A decimal counter has _____ states.<br>(a) 5      (b) 10      (c) 15      (d) 20  | 1     | K1      | CO3 |
| 7. The analysis of Asynchronous sequential circuits is used to obtain _____.<br>(a) A table      (b) A diagram      (c) Graph      (d) Flowchart   | 1     | K1      | CO4 |
| 8. In a combinational circuit, if the outputs before and after change of input are the same then the hazard is called a _____.<br>(a) Static Hazard      (b) Dynamic Hazard      (c) Essential Hazard      (d) Static 1 Hazard | 1     | K1      | CO4 |
| 9. EPROM contents can be erased by exposing it to _____.<br>(a) UV rays      (b) Infrared rays<br>(c) Burst of microwaves      (d) Intense heat radiations   | 1     | K1      | CO5 |
| 10. Which keyword is commonly used in Verilog to declare a behavioral block of code?<br>(a) always      (b) assign      (c) module      (d) reg  | 1     | K1      | CO6 |

**PART - B (12 × 2 = 24 Marks)**

Answer ALL Questions

- |  |   |    |     |
|--|---|----|-----|
| 11. Convert $(0.6875)_{10}$ to binary.                               | 2 | K2 | CO1 |
| 12. Define odd and even parity.                                      | 2 | K1 | CO1 |
| 13. What are Universal Gates? Why are they named so?                 | 2 | K1 | CO2 |
| 14. Differentiate between encoder and decoder.                       | 2 | K2 | CO2 |
| 15. Define Ripple counter.   | 2 | K1 | CO3 |
| 16. Differentiate between latches and flip flop.                     | 2 | K2 | CO3 |
| 17. Compare the critical race and non-critical race                  | 2 | K2 | CO4 |
| 18. Define a primitive flow table.                                   | 2 | K1 | CO4 |
| 19. Define combinational PLD.  | 2 | K1 | CO5 |
| 20. Compare DRAM and SRAM.   | 2 | K2 | CO5 |
| 21. Name the modeling techniques available in HDL.                   | 2 | K1 | CO6 |
| 22. Write the VHDL code for a 1X2 demux using behavioural modelling. | 2 | K2 | CO6 |

**PART - C (6 × 11 = 66 Marks)**

Answer ALL Questions

23. a) i) Convert  $(725.25)_8$  to its decimal, binary and Hexadecimal equivalent. 6 K2 CO1  
ii) Interpret the 1's and 2's Complement of 8-digit binary number 10101101. 5 K2 CO1
- OR**
- b) Explain in detail about Excess-3 and Gray code. 11 K2 CO1
24. a) Design a 4 bit BCD to Excess-3 code converter. 11 K3 CO2
- OR**
- b) Design Full subtractor and derive expression for difference and borrow. Realize using two half subtractor. 11 K3 CO2
25. a) Design a synchronous counter with the following sequence: 0, 1, 3, 7, 6, 4 and repeats. Use JK Flip flop. 11 K3 CO3
- OR**
- b) Examine the operation of master slave flip flop and show how the race around condition is eliminated in it. 11 K3 CO3
26. a) Explain the steps for the design of asynchronous sequential circuits with an example. 11 K2 CO4
- OR**
- b) Discuss in detail the procedure for reducing the flow table with an example. 11 K2 CO4
27. a) Solve to implement the two following Boolean functions using 8X2 PROM  $F1 = \sum m(3,5,6,7)$ ,  $F2 = \sum m(1,2,3,4)$ . 11 K3 CO5
- OR**
- b) Implement the following function using PLA:  $A(X,Y,Z) = \sum m(1,2,4,6)$ ,  $B(X,Y,Z) = \sum m(0,1,6,7)$ ,  $C(X,Y,Z) = \sum m(2,6)$  11 K3 CO5
28. a) Summarize in detail the concept of structural modeling in HDL with an example of half subtractor. 11 K2 CO6
- OR**
- b) Summarize in detail the concept of structural modeling in HDL with an example of half adder. 11 K2 CO6