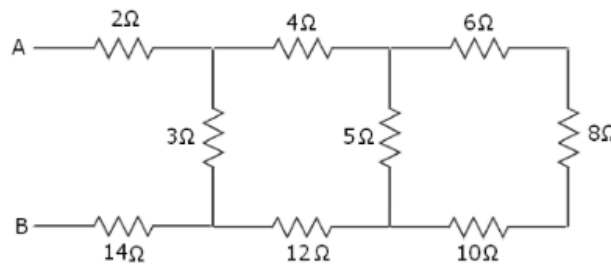


- | | | | |
|---|---|----|-----|
| 17. Define damping ratio. Give the damping ratio expressions for RLC series circuit. | 2 | K1 | CO3 |
| 18. Distinguish between natural and forced response. | 2 | K2 | CO3 |
| 19. Find the coupling coefficient if the mutual inductance is 20H, the inductance of coil 1 is 2H and the inductance of coil 2 is 8H. | 2 | K2 | CO4 |
| 20. An RLC circuit has a resonance frequency of 160 kHz and a Q-factor of 100. Calculate the band width. | 2 | K2 | CO4 |
| 21. Mention the advantages of three phase system over single phase system. | 2 | K2 | CO5 |
| 22. Indicate the expression for real, reactive, apparent power and power factor in a three phase AC circuit. | 2 | K2 | CO5 |

PART - C (6 × 11 = 66 Marks)


Answer ALL Questions

23. a) Determine the total power consumed by the supply when 100 V is applied across A and B shown in Fig. 11 K3 CO1




OR

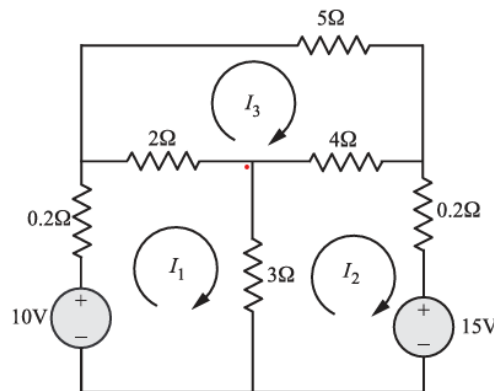- b) For the electrical network shown in Fig. determine the loop currents and all branch currents. 11 K3 CO1




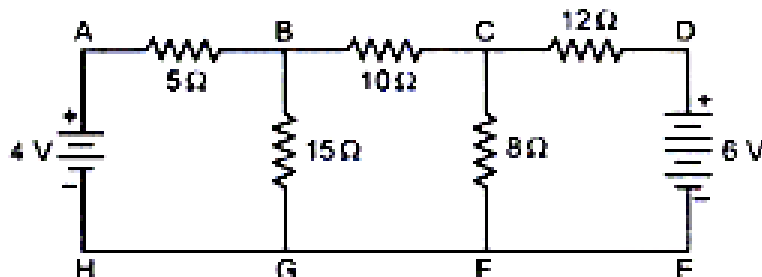24. a) Apply Thevenin's theorem calculate the current through 10 Ω resistor for the given circuit Fig. 11 K3 CO2



OR

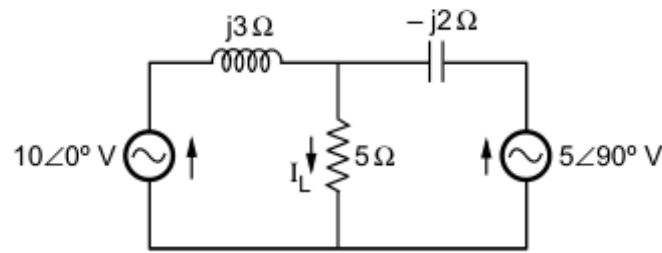
- b) Determine the current flowing through branch I_L of the given network Fig. using Norton's theorem. 11 K3 CO2



25. a) Determine the transient current expression of the RL transient circuit with DC excitation. 11 K3 CO3

OR

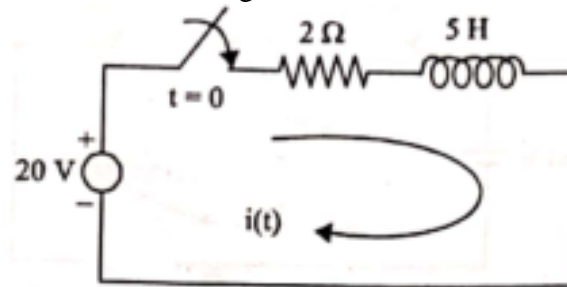- b) In a circuit shown in figure Fig. determine the expression for transient current after the switch is closed at $t = 0$, assuming zero initial conditions. 11 K3 CO3



26. a) Derive an expression for Resonant frequency, Q - Factor, bandwidth and half power frequency for a RLC series resonance circuit 11 K3 CO4

OR

- b) Solve the series RLC circuit parameters with $R = 15 \Omega$, $L = 0.54 \text{ H}$ and $C = 40 \mu\text{F}$ has an applied voltage of 150 V at resonant frequency. Find the resonant frequency, quality factor, upper and lower half power frequencies, bandwidth, current at resonance, current at half-power points and voltage across the inductance at resonance. 11 K3 CO4

27. a) Illustrate and discuss the steps involved in calculating power for a three-phase circuit using the two-wattmeter method. 11 K3 CO5

OR

- b) Each phase of a three-phase alternator generates a voltage as 3500 volts and Carries a Maximum Current of 250 amps. Analyze the given data find the line current, line voltage and total kVA Capacity if (i) Delta connected (ii). Star connected. 11 K3 CO5

28. a) (i) Explain briefly about the concept of parallel resonance. 6 K2 CO4
(ii) Discuss in detail about the three phase 3-wire circuits with star connected balanced loads. 5 K2 CO5

OR

- b) (i) Explain in detail in the concept of co-efficient coupling. 6 K2 CO4
(ii) Three inductive coils each having resistance of 16Ω and reactance of 12Ω are connected in star across a 400V, three-phase 50 Hz supply. Calculate: (i) line current (ii) line voltage. 5 K2 CO5